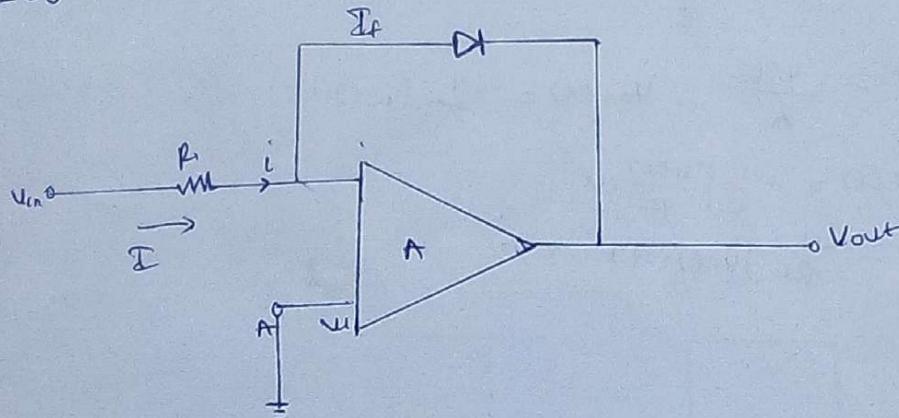


### QUESTION 1

Draw the circuit diagram and derive the expression for the closed loop gain of Op-Amp Configured as

- (i) Logarithm Amplifier (ii) Anti-Log Amplifier (iii) Integrator
- (iv) Non-Inverting Amplifier (v) Differentiator

#### LOGarithm Amplifier




$$V_m = IR, \quad I = \frac{V_m}{R}, \quad I = If$$

$$If = \ln\left(\frac{V_D}{e^{NVT}} - 1\right) = I_0 \left[ \frac{V_D}{e^{NVT}} \right] \quad \text{or} \quad \frac{V_D}{I_0 NVT} = \ln\left(\frac{If}{I_0}\right)$$

$$V_D = \mu k T \ln\left(\frac{If}{I_0}\right), \quad V_D = -V_o \quad \text{and} \quad I = If = \frac{V_m}{R}$$

$$V_{out} = NVT \ln\left(\frac{V_m}{R I_0}\right)$$

#### (ii) Anti-Log Amplifier

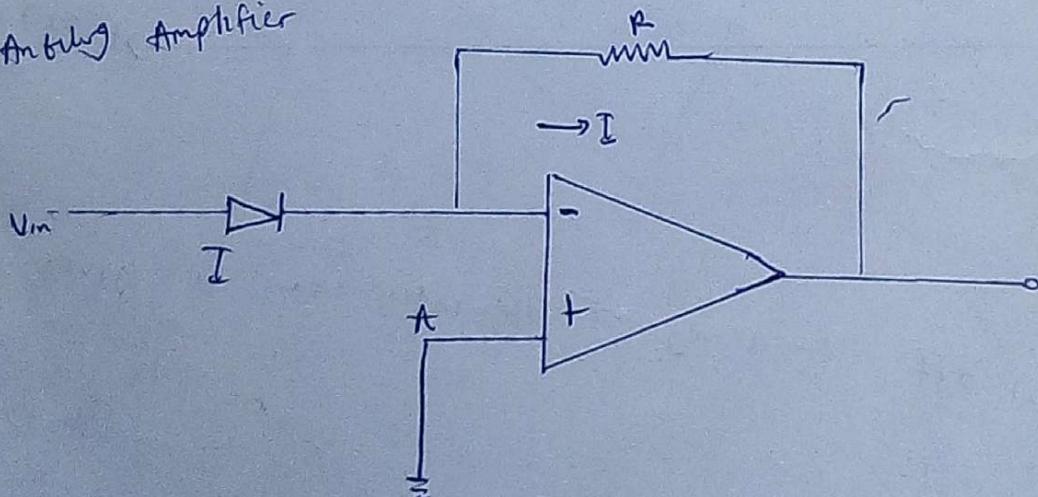


$$I = I_0 \left( \frac{V_D}{e^{NVT}} - 1 \right) = I_0 e^{\frac{V_D}{NVT}} \quad V_D = V_m$$

$$\text{and } V_{out} = -If \times R, \quad If = -\frac{V_m}{R}, \quad V_{out} = -I_f R$$

$$V_{out} = -R I_0 e^{\left(\frac{V_m}{NVT}\right)}$$



(W) INTEGRATOR

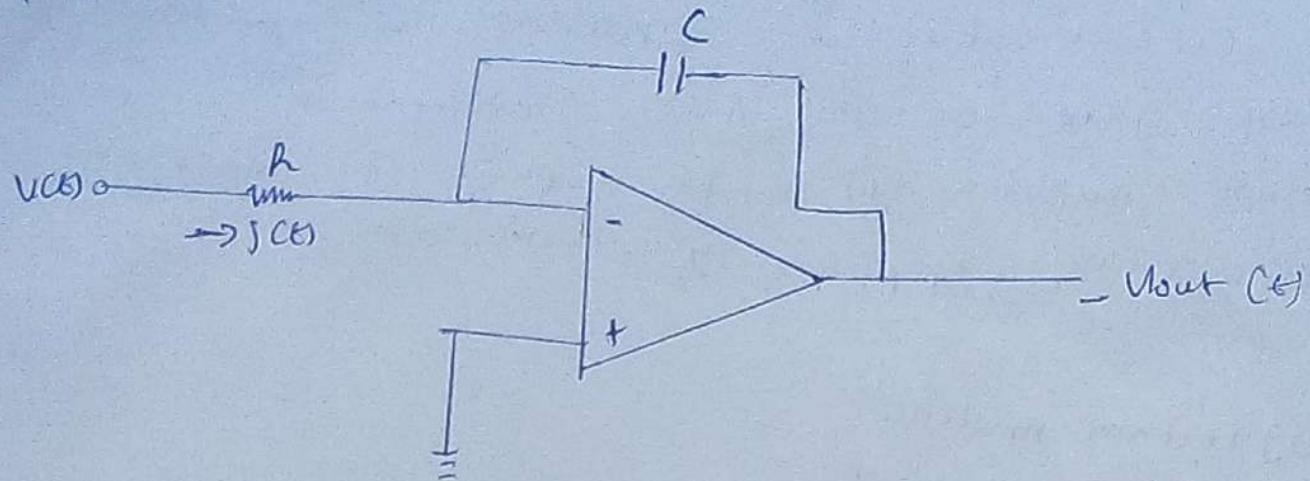

$$i(t) = \frac{V(t)}{R}, \quad V_{out}(t) = -\frac{1}{C} \int i(t) dt$$

$$V_{out}(t) = -\frac{1}{C} \int \frac{V(t)}{R} dt$$

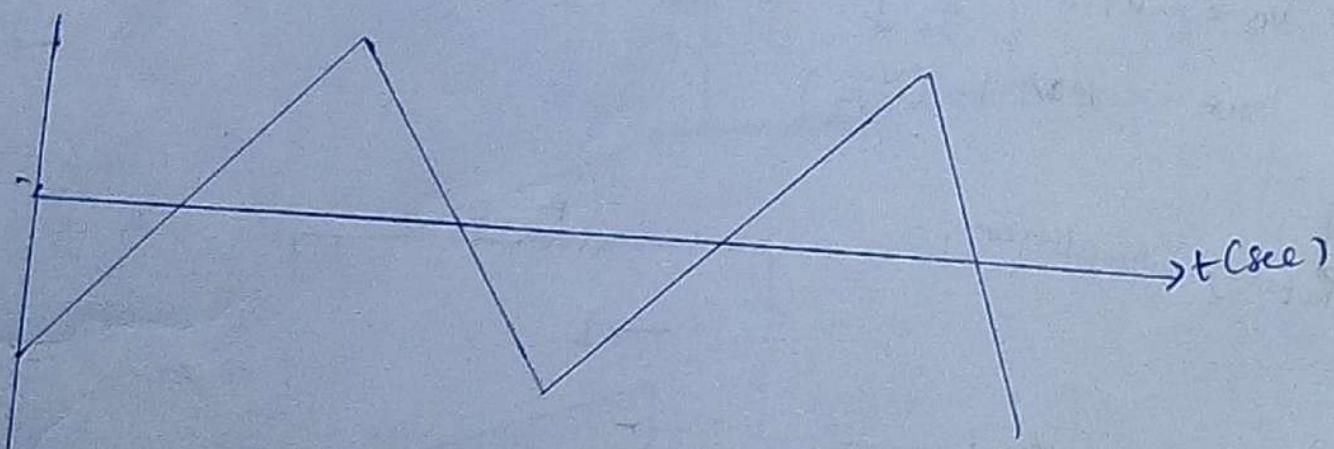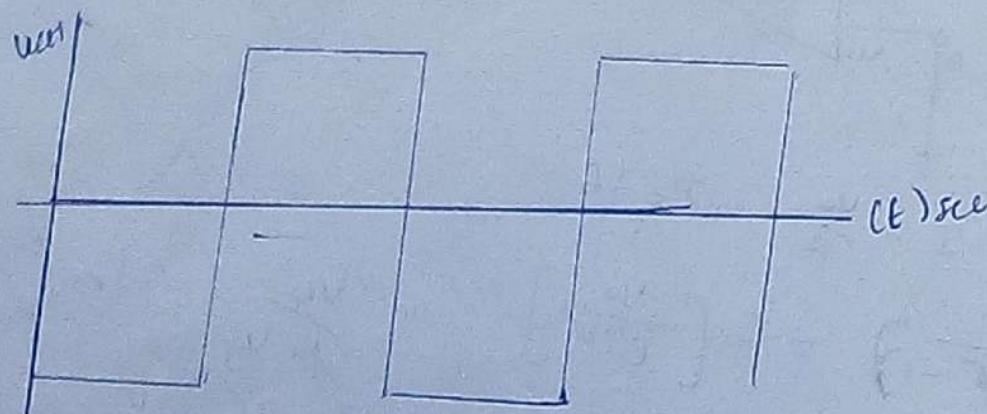
$$V_{out} = -\frac{1}{RC} \int V(t) dt + A$$



The cut off frequency of the integrator is given by

$$f_c = \frac{1}{2\pi RC}$$

# INVERTING AMPLIFIER

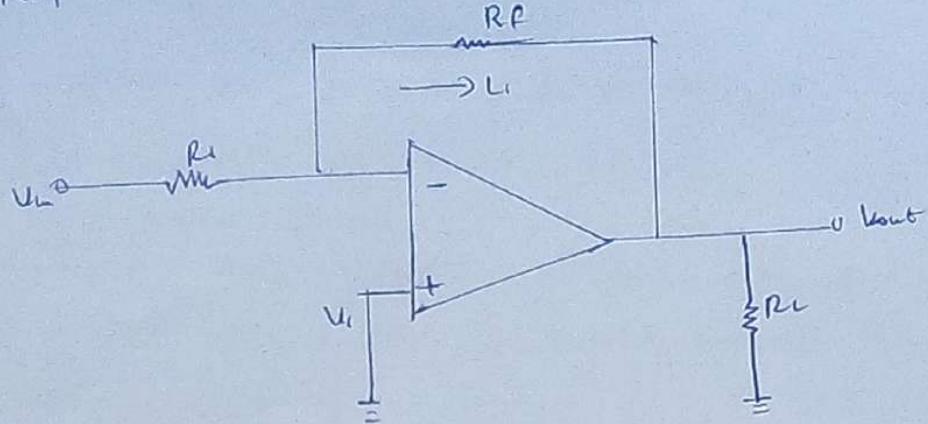


$$\frac{V_{in} - V_2}{R_1} = \frac{V_2 - V_{out}}{R_f}$$

$V_2 = 0$  because of virtual ground

$$\frac{V_{in}}{R_1} = -\frac{V_{out}}{R_f}, \quad \frac{V_{out}}{V_{in}} = A_f = -\frac{R_f}{R_1}$$

$$V_{out} = -\frac{R_f}{R_1}(V_{in})$$

## DIFFERENTIATOR

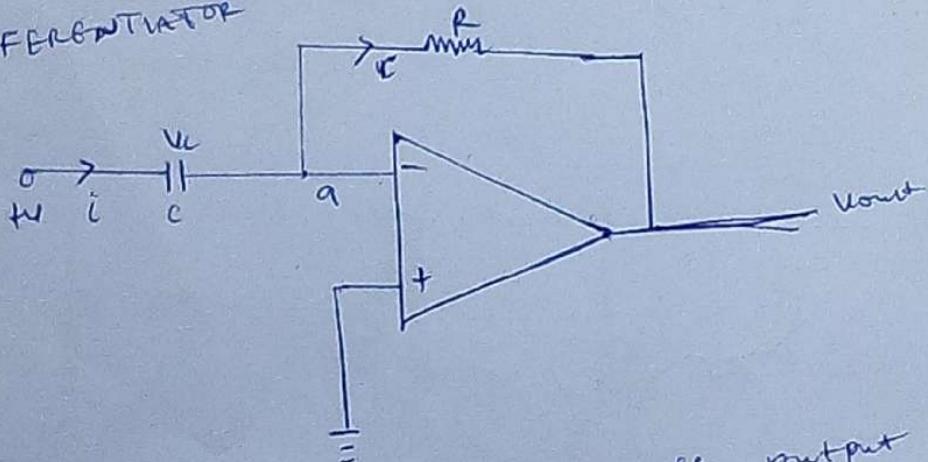

The differentiator is a circuit whose output is proportional to the rate of change of its input signal.

Let  $i$  be the rate of change of charge

$$i = \frac{dq}{dt}$$

$$i = \frac{dq}{dt} = \frac{d(CV_c)}{dt} = C \frac{dV_c}{dt}$$


$$V_{out} = -IR = -\left[C \frac{dV_c}{dt}\right] R$$

$$V_{out} = -CR \frac{dV_c}{dt}$$

Question 2

Fig below shows the circuit diagram of a two stage RC coupled amplifier.

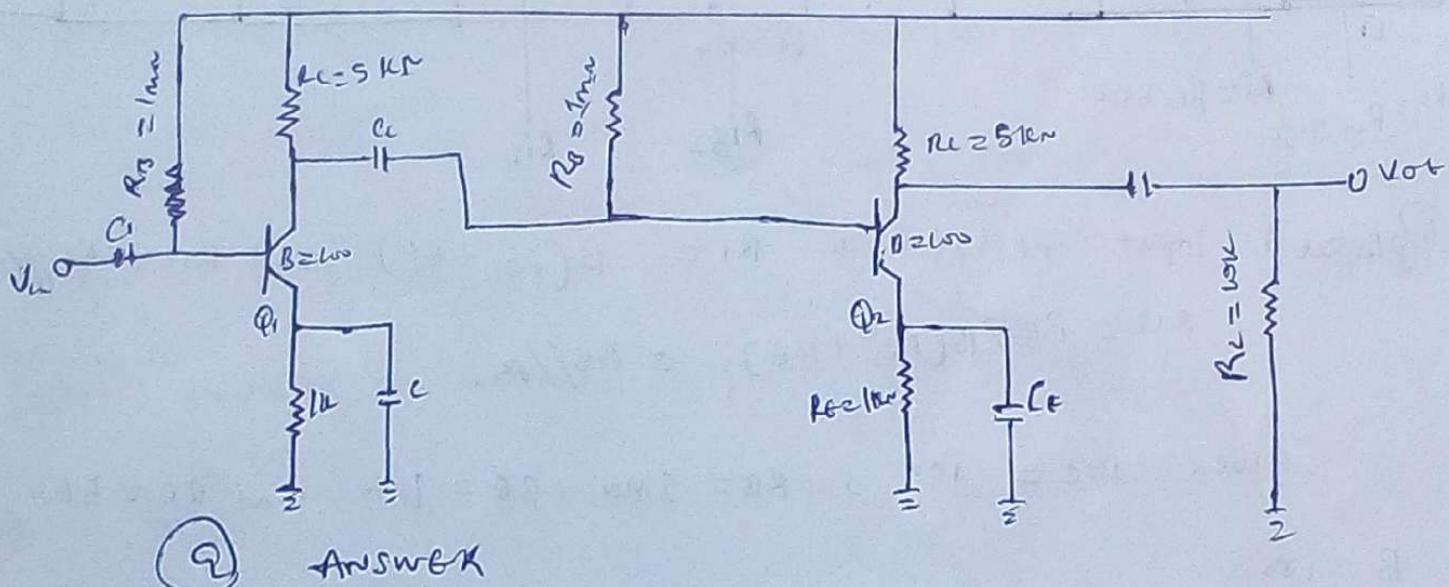
- Draw the DC and AC equivalent circuit
- Determine the value of the
- Input resistance (iii) Output resistance (iv) Current gain (v) Voltage gain for first stage and second stage (vi) Overall voltage gain (vii) Overall dB voltage gain




Q

ANSWER

DC equivalent circuit

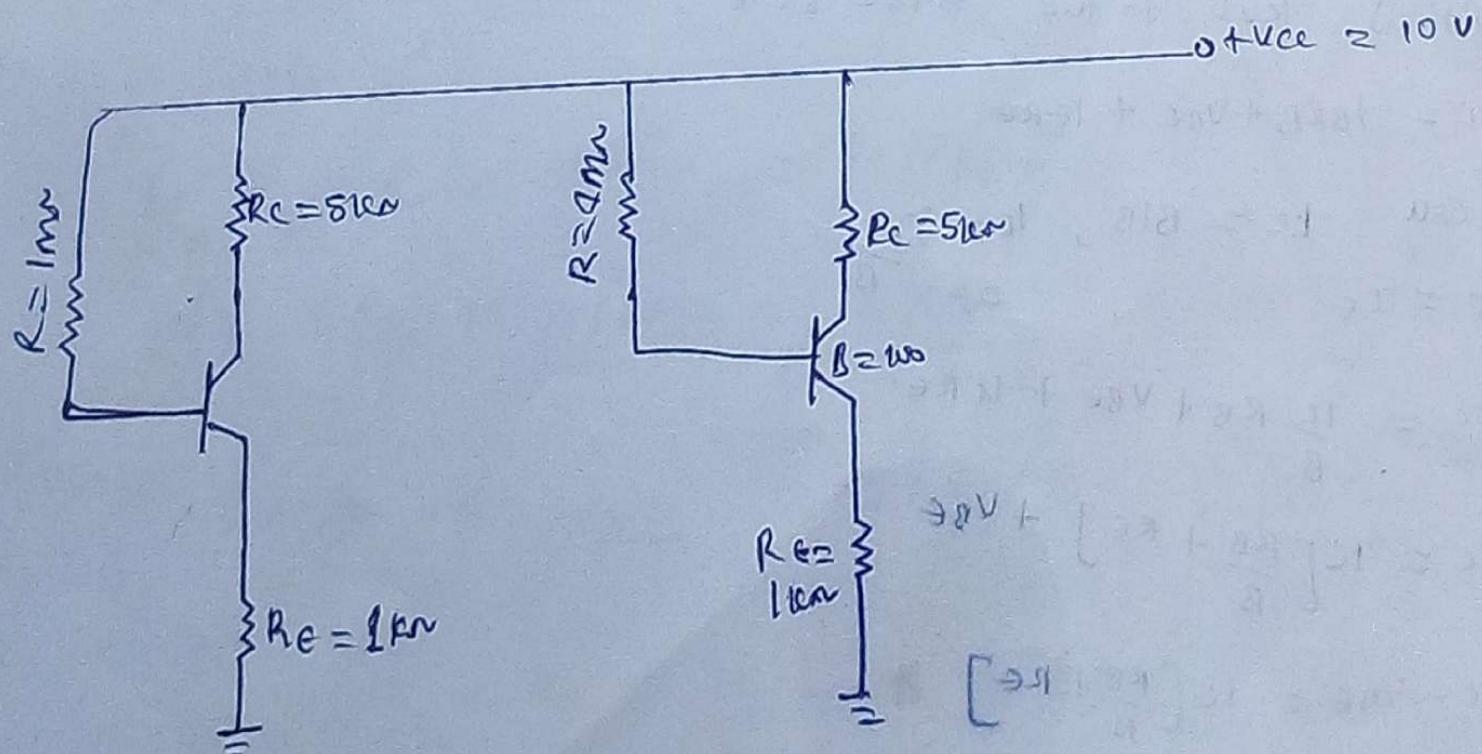

AC Circuit Equivalent

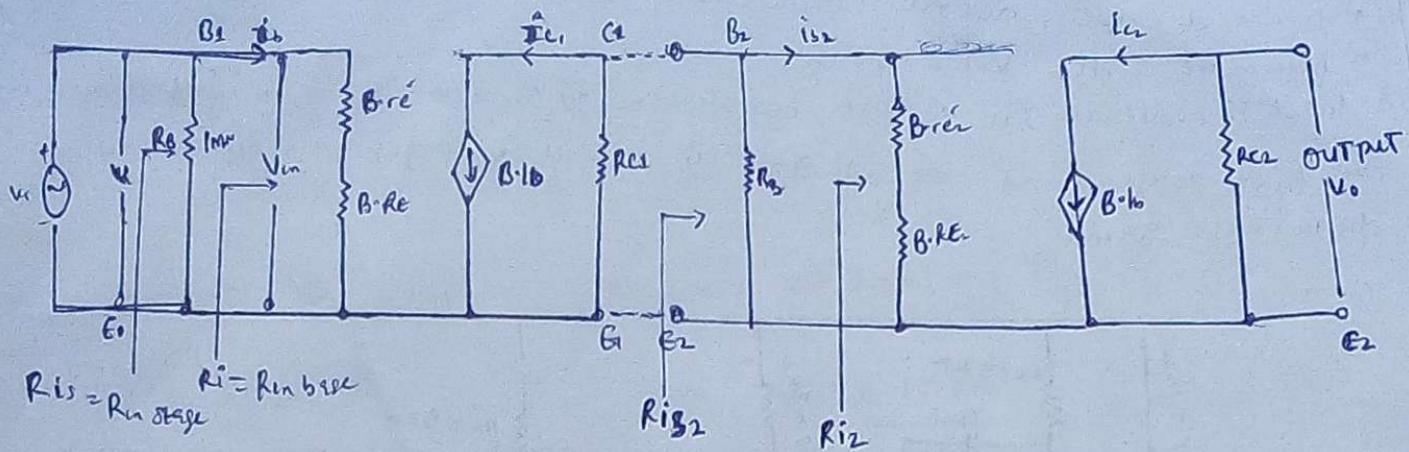

$$R_{IS} = R_B \parallel R_{FB}$$

(b) ~~Step 1~~ Input resistance  $R_I = B(r_e + R_E)$  and  $R_{IS} = R_B \parallel (B(r_e + R_E))$

$$R_{IS} = R_B \parallel B(r_e + R_E) = R_B \parallel R_i$$

Given  $V_{CC} = 10V$ ,  $R_B = 1MN$ ,  $R_E = 1k\Omega$  and  $R_C = 5k\Omega$

$$B = 100$$

First stage input resistance

Applying KVL to the base side

$$V_{CC} = I_B R_B + V_{BE} + I_C R_E$$

$$\text{recall } I_C = B I_B, I_B = \frac{I_C}{B}$$

$$I_C \approx I_E$$

$$V_{CC} = \frac{I_C}{B} R_B + V_{BE} + I_C R_E$$

$$V_{CC} = I_C \left[ \frac{R_B}{B} + R_E \right] + V_{BE}$$

$$V_{CC} - V_{BE} = I_C \left[ \frac{R_B}{B} + R_E \right]$$

$$I_C = \frac{V_{CC} - V_{BE}}{\frac{R_B}{B} + R_E} \approx I_E$$

$$\frac{R_B}{B} + R_E$$

$$I_E = \frac{I_O - 0.7}{\frac{1 \times 10^6}{100} + 1 \times 10^3} = \frac{9.3}{11000} = 0.85mA$$

$$r_e = \frac{25mV}{I_E} = \frac{25 \times 10^{-3} V}{0.85 \times 10^{-3} A} = \frac{25}{0.85} = 29.411 \Omega$$

Input resistance  $R_i = B(r_e + R_E)$

$$R_i = 100 [29.411 + 1k] = 102941.17 \Omega = 102.94 k\Omega$$

Since  $R_E \gg r_e$  I can neglect  $r_e$

$$R_i \approx B(R_E) = 100(1k) = 100k\Omega$$

$$R_{IS} = R_B // R_i = \frac{R_B \times R_i}{R_B + R_i} = \frac{1 \times 10^6 \times 100 \times 10^3}{1 \times 10^6 + 100 \times 10^3} = 90.909.09 \Omega$$

$$R_{IS} = 90.909 k\Omega$$

Input resistance for the stage =  $90.909 k\Omega$

For first and second stage  $R_i \approx 100k\Omega$  and  $R_{IS} = 90.909 k\Omega$

(v) Output resistance

Input resistance of the second stage is the load for the first stage

$$R_o \text{ for first stage} = R_C // R_{IS2}$$

$$R_o = 5k // 90.909 k\Omega = \frac{5 \times 90.909}{5 + 90.909} = 4.739 k\Omega$$

$$\text{Second stage } R_o = R_C // R_L = 5k // 10k\Omega = \frac{5 \times 10}{5 + 10} = 3.33 k\Omega$$

(vi) current gain  $A_i = \frac{I_C}{I_B} = B = 100$

(vii) voltage gain for First stage

$$A_v = \frac{R_o}{r_{e1}} = \frac{4.739 k\Omega}{29.411} = 161.13$$

$$\text{Second stage, voltage gain } A_v = \frac{R_{o2}}{r_{e1}} = \frac{3.33 k\Omega}{29.411} = 113.22$$

$$(v) \text{ overall voltage gain} = A_{v1} \times A_{v2} = 161.3 \times 113.22 \\ = 18251.54$$

(vi) overall dB voltage gain

$$\text{power gain} = 10 \log_{10} \frac{P_{\text{out}}}{P_{\text{in}}} \text{ dB}$$

$$P_1 = \frac{V_{\text{in}}^2}{R}; P_2 = \frac{V_{\text{out}}^2}{R}$$

$$\text{Voltage gain in dB} = 10 \log_{10} \frac{V_{\text{out}}^2/R}{V_{\text{in}}^2/R} = 20 \log_{10} \frac{V_{\text{out}}}{V_{\text{in}}}$$

for multistage amplifier

$$\text{Gain} = \frac{V_2}{V_1} \times \frac{V_3}{V_2}$$


$$\text{Gain in dB} = 20 \log_{10} \frac{V_2}{V_1} \times \frac{V_3}{V_2}$$

$$= 20 \log_{10} \frac{V_2}{V_1} + 20 \log_{10} \frac{V_3}{V_2}$$

$$\text{Voltage gain in dB} = 20 \log_{10} [161.3] + 20 \log_{10} [113.22] = \\ = 44.153 + 41.077 = 85.23$$
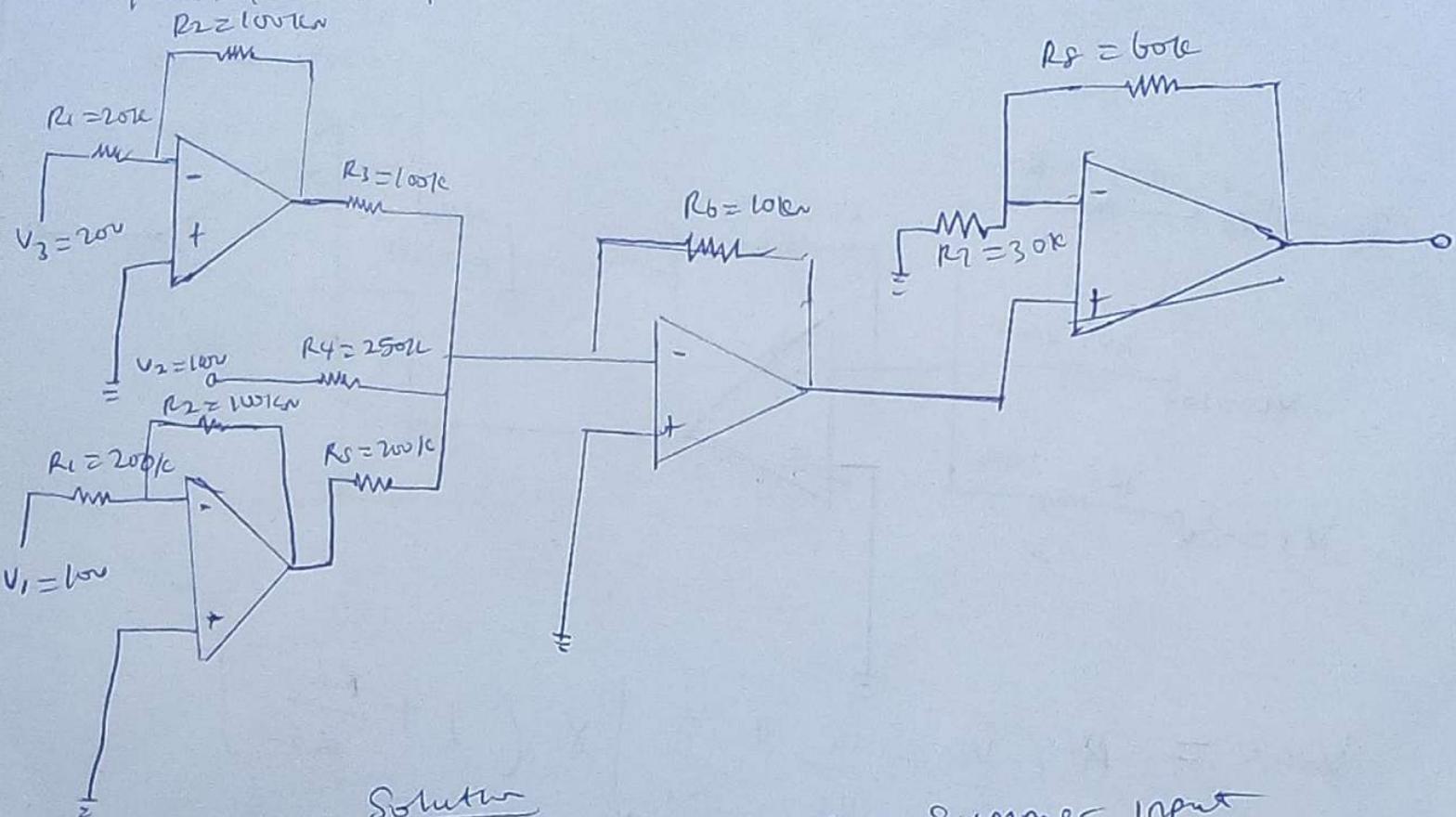
### Question 3

Find the output of the multistage Amplifier



#### Solution

Let compute for  $V_{in}$  at the Summer input



$V_{out}$  for the first stage

$$V_{out} = -\frac{100}{200} \times 10 = -5V \quad \hat{=} V_1$$

Second stage  $V_{out}$

$$V_{out} = -\frac{100}{20} \times 20 = -100V \quad \hat{=} V_3$$

redraw the stages

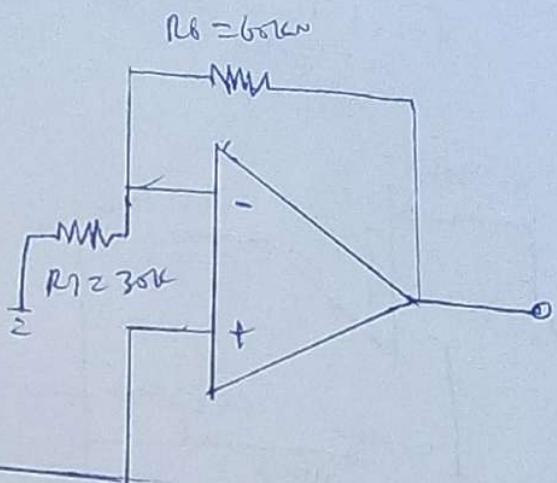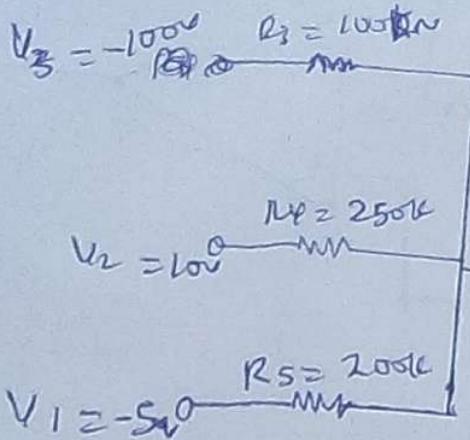

$$V_{out} = A_f \left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right] \times \left( 1 + \frac{R_6}{R_7} \right)$$


$$= 10 \left[ \frac{-5}{200} + \frac{10}{250} - \frac{100}{100} \right] \times \left[ 1 + \frac{60}{30} \right]$$

$$= 10 \left[ \frac{-1}{40} + \frac{1}{25} = 1 \right] \times [3]$$

$$= 10 \left[ -\frac{197}{200} \right] \times 3 = -29.55V$$

QUESTION ④

- a) find  $I_C$ ,  $V_{CE}$  and draw the load line on output character  
and indicate the Q-point for the circuit of fig below  
take  $V_{BE} = 0.7V$  and  $B = 50$

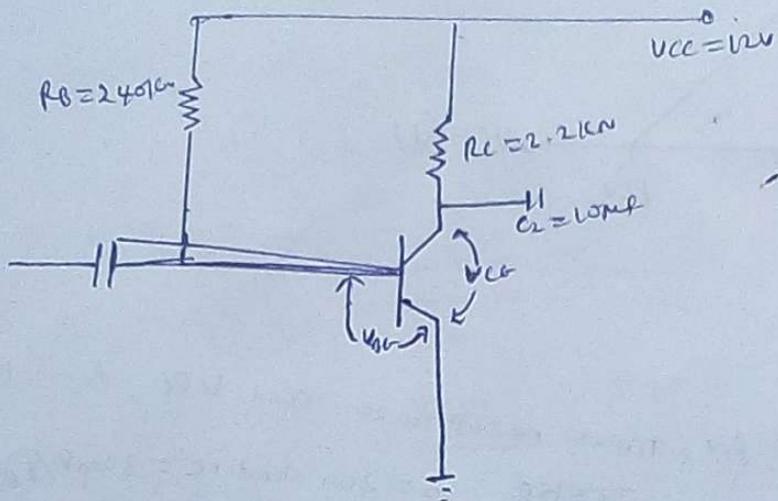Solution

$$V_{CC} = 12V, R_B = 240k\Omega, R_C = 2.2k\Omega$$

DC load line,  $V_{CE} = V_{CC} - I_C R_C$  when  $I_C \approx 0$   $V_{CE} = V_{CC} = 12V$   
whence  $V_{CE} = 0$   $V_{CE} = I_C R_C$   $I_C = \frac{V_{CC}}{R_C} = \frac{12}{2.2k} = 5.45mA$

The operating point Q,  $V_{BE} = 0.7$

Applying KVL to base side


$$I_B R_B + V_{BE} = V_{CC}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 - 0.7}{240k} = 0.47mA$$

Collector current  $I_C = B I_B = 50 \times 0.47mA = 2.354mA$


~~$I_C = 2.354mA$~~
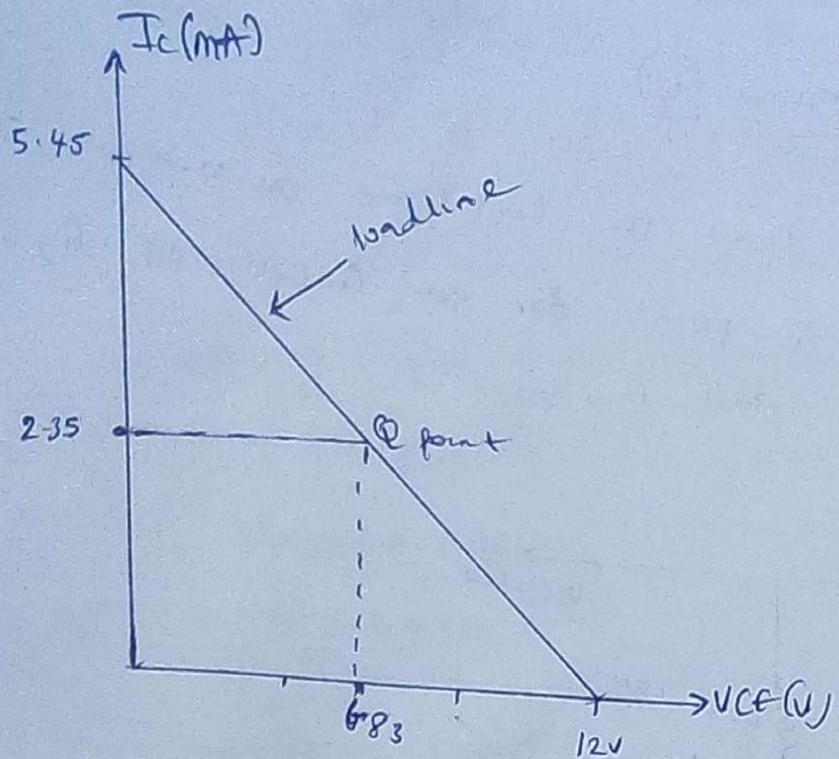
$$\begin{aligned} V_{CE} &= V_{CC} - I_C R_C \\ &= 12 - (2.354 \times 10^{-3} \times 2.2 \times 10^3) \\ &= 12 - 5.17 = 6.83V \end{aligned}$$



(4b)

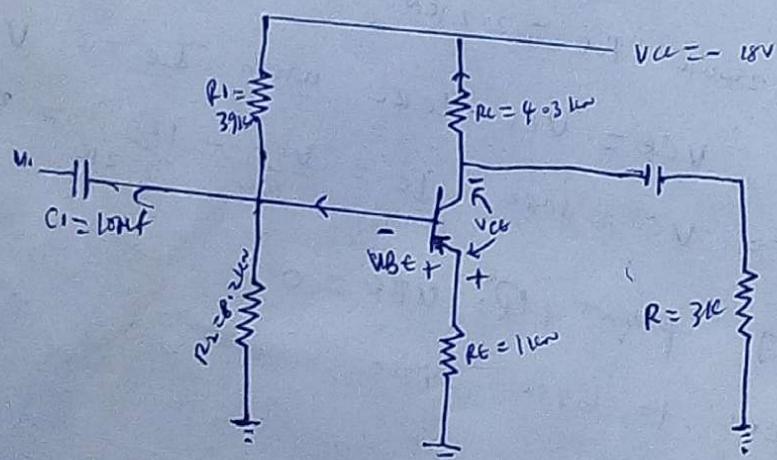Find the voltage gain  $A_v$ , input resistance and  $V_{CE}$  for the amplifier of fig below. Take  $\beta = 200$  and  $r_e = 30mV/I_E$



Solution

$$\beta = 200$$

$$r_e = 1k\Omega$$

$$V_{CE} = -18V$$

The negative indicates that collector is connected in reverse bias (PnP)

Let compute for  $I_E$

$$\text{Voltage across } R_2, V_2 = \frac{V_{CE}}{R_1 + R_2} \times R_2 = \frac{18}{39k\Omega + 8.2k\Omega} \times 8.2k\Omega$$

$$V_2 = 3.127V$$

Applying KVL to the base side

$$-V_2 + V_{BE} + I_E R_E = 0$$

$$V_2 - V_{BE} = I_E R_E$$

$$I_E = \frac{V_2 - V_{BE}}{R_E}$$

$$I_E = \frac{V_2 - V_{BE}}{R_E}$$

$$= \frac{3.127 - 0.7}{1k} = 2.427mA$$

$$r_e' = \frac{30mV}{I_E} = \frac{30mV}{2.427mA} = 12.36\Omega$$

$$\text{Input resistance} = \beta(r_e' + R_E)$$

Since  $R_E \gg r_e'$

$$r_i = \beta R_E = 200 \times 1k = 200k$$

$$\text{Input resistance } r_i = 200k$$

$$\text{Voltage gain} = \frac{R_C}{r_e'}$$

$$R_{AC} = r_e' / R_C = 3k / 4.3k = \frac{3 \times 4.3}{4.3 + 300} = 1.77k\Omega$$

$$\text{Voltage gain } A_v = \frac{R_{AC}}{r_e'} = \frac{1.77k}{12.36} = 142.97$$

### Question (5)

V<sub>CE</sub>

Applying KVL at collector side

$$V_{CE} = -V_{CC} + I_E (R_C + r_e)$$

$$= -V_{CC} + [2.427mA [4.3k + 1k]]$$

$$= -V_{CC} + [2.427(5.3)]$$

$$V_{CE} = -V_{CC} + [12.863]$$



$$= -18 + 12.863$$

$$V_{CE} = -5.1369V$$

negative sign shows that collector emitter voltage is connected in ~~reverse~~ reverse bias.

QUESTION (5)

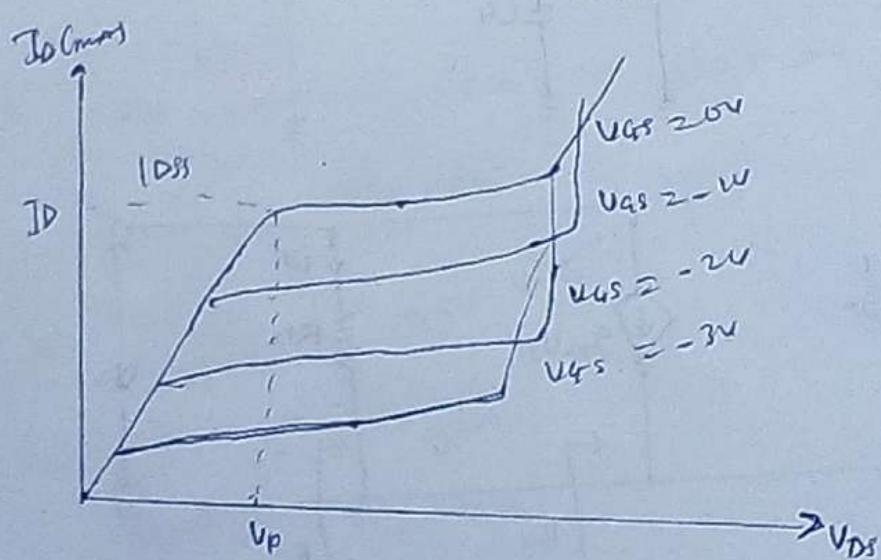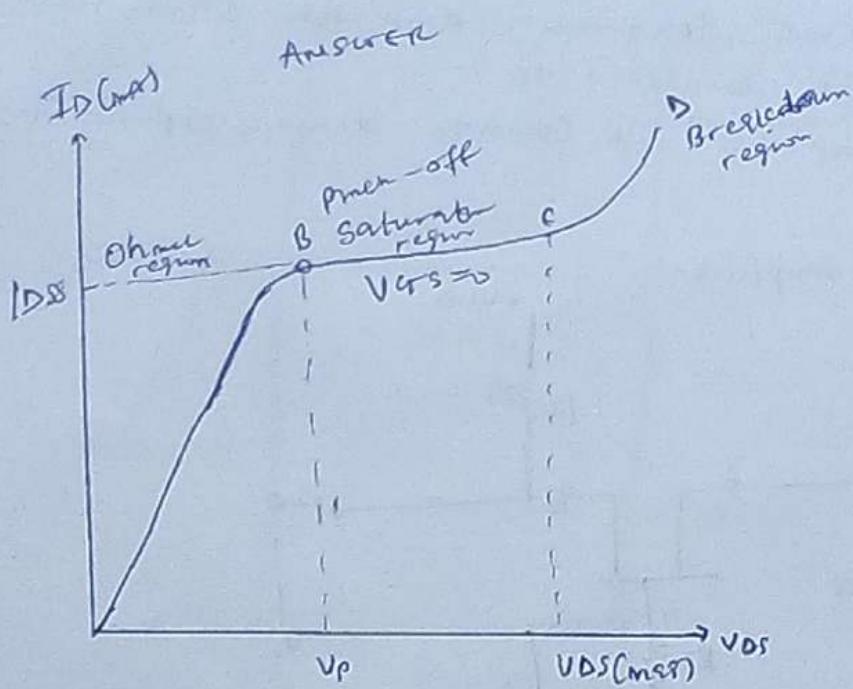a) Draw the graph showing the drain characteristic of JFET with  $V_{GS} = 0V$  and explain briefly the different regions in the curve.



- (i) Ohmic region: The drain current increases linearly with the inverse in drain to source voltage

- (ii) Curve AB: The drain current follows at the reverse square law ~~rate~~ rate with increased in drain to source voltage

- (iii) Pinch off region: The drain current remain constant at its maximum value  $ID_{SS}$ , the drain current ~~is~~ the pinch off region depend upon the gate to source voltage and is given by



$$ID = ID_{SS} \left[ 1 - \frac{V_{GS}}{V_p} \right]_{\text{Pinch off}}$$

iii) Breakdown region: the drain current increase rapidly as the drain to source voltage is increased.


(5b)

Draw the circuit diagram and the equivalent circuit of N channel JFET connected as  
 ① Common gate amplifier ② Common drain amplifier ③ Common source

Common gate Amplifier

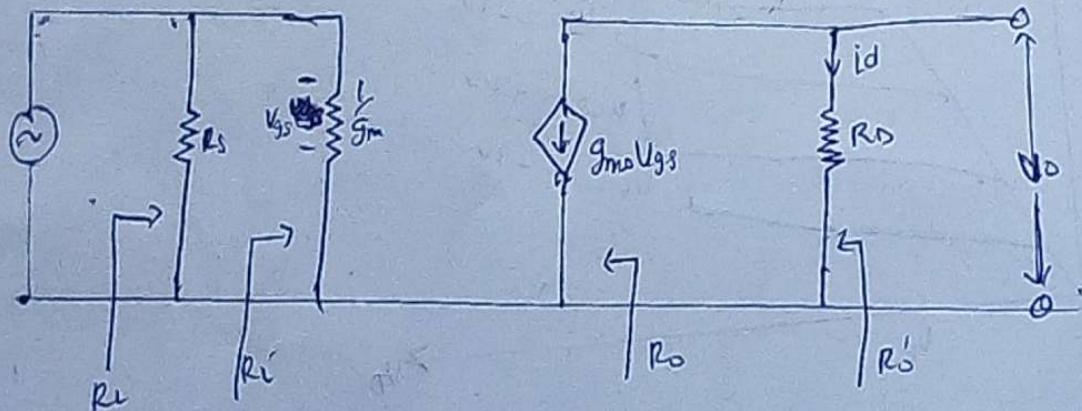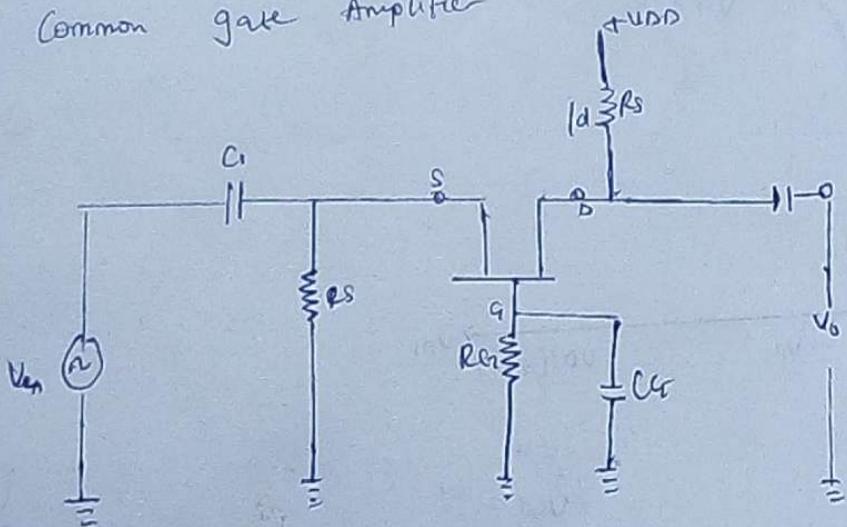


④ Common drain amplifier

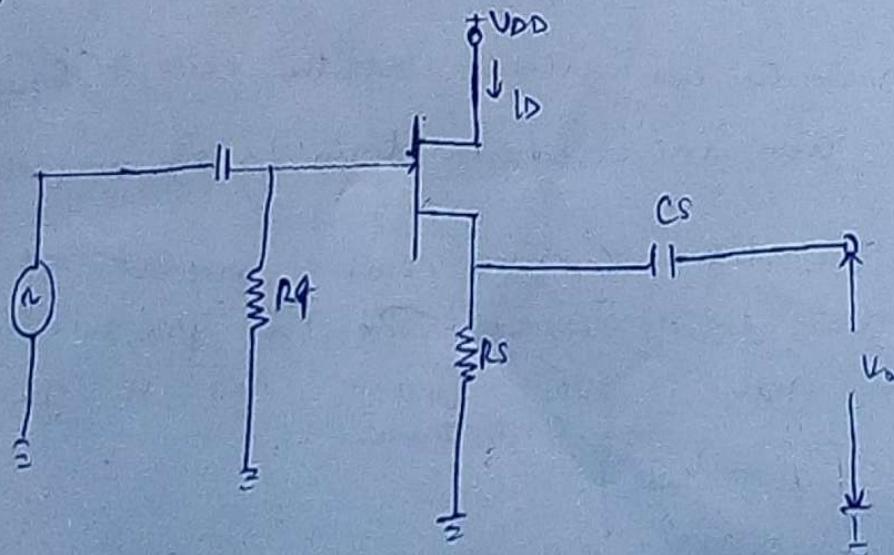

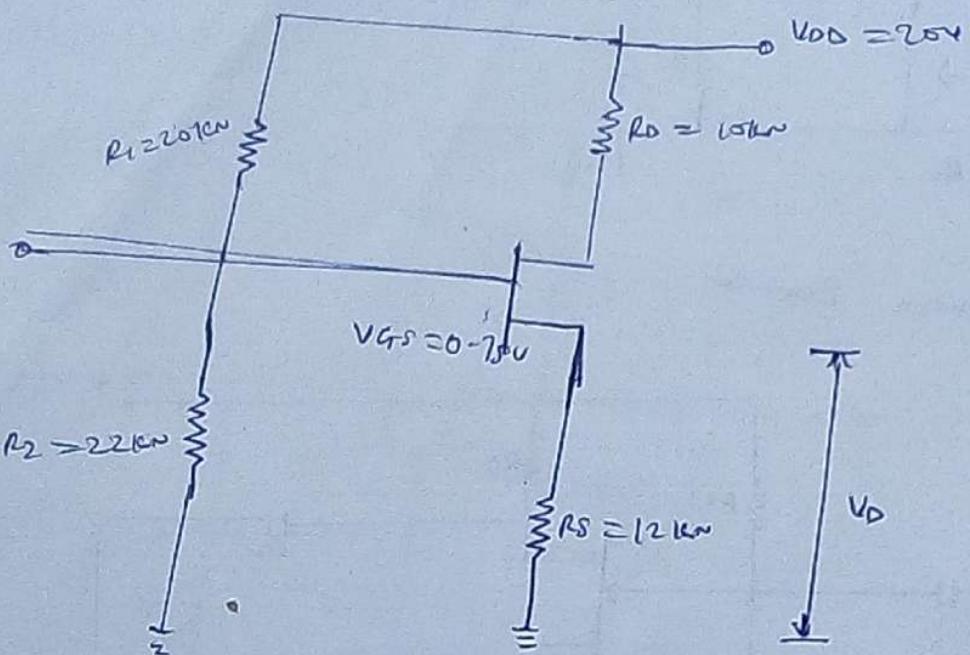Question 6

- ② Calculate the drain current  $I_D$  and drain voltage  $V_D$  for the circuit below



Solution

$$R_1 = 20 \text{ k}\Omega, R_2 = 22 \text{ k}\Omega, V_{GS} = 0.75 \text{ V}, V_{DD} = 20 \text{ V}, R_D = 10 \text{ k}\Omega \text{ and } R_S = 12 \text{ k}\Omega$$

$$V_2 = V_G = \frac{V_{DD}}{R_1 + R_2} \times R_2$$

$$V_2 = \frac{20}{20+22} \times 22 = 10.48 \text{ V}$$

KVL at the gate

~~$$V_{GS} = V_2 - I_D R_S$$~~


$$V_2 - V_{GS} = I_D R_S$$

$$I_D = \frac{V_2 - V_{GS}}{R_S}$$



$$I_D = \frac{10.48 - 0.75}{12 \text{ k}\Omega} = 0.81 \text{ mA}$$

$$V_D = I_D R_D = 0.81 \text{ mA} \times 10 \text{ k}\Omega = 8.1 \text{ V}$$

$$V_D = 8 \text{ V}$$

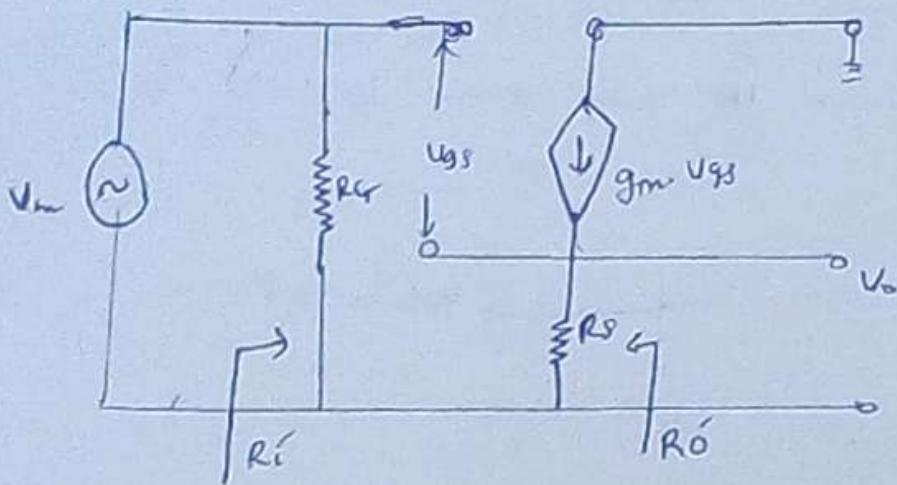


(ii) Common Source

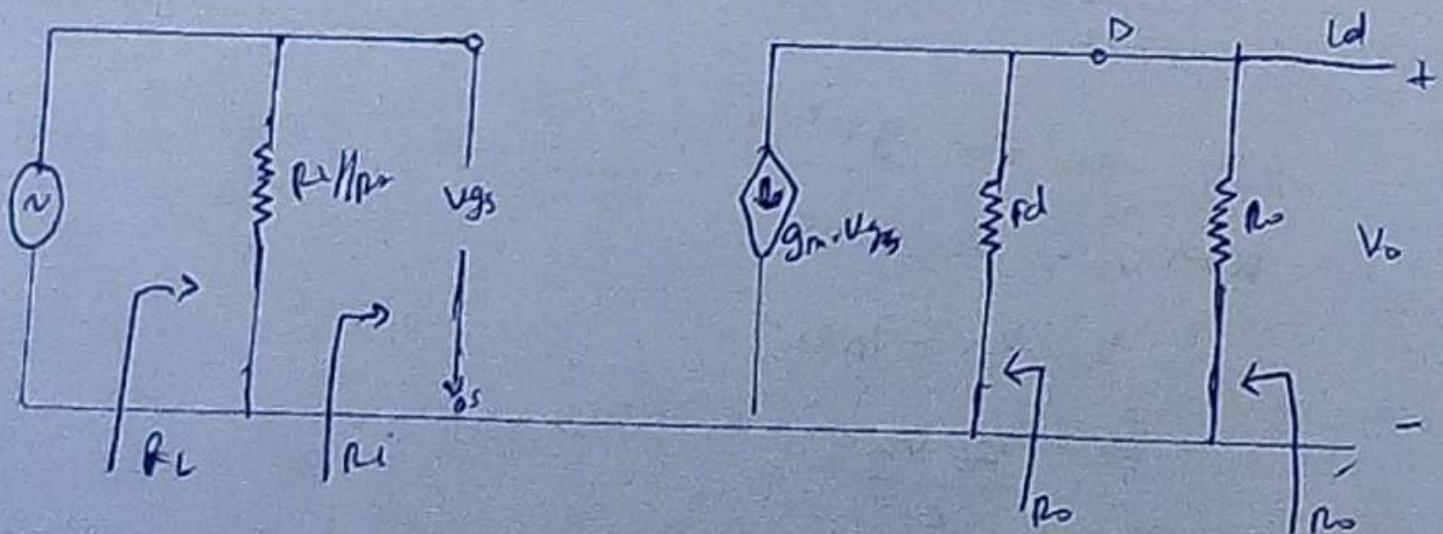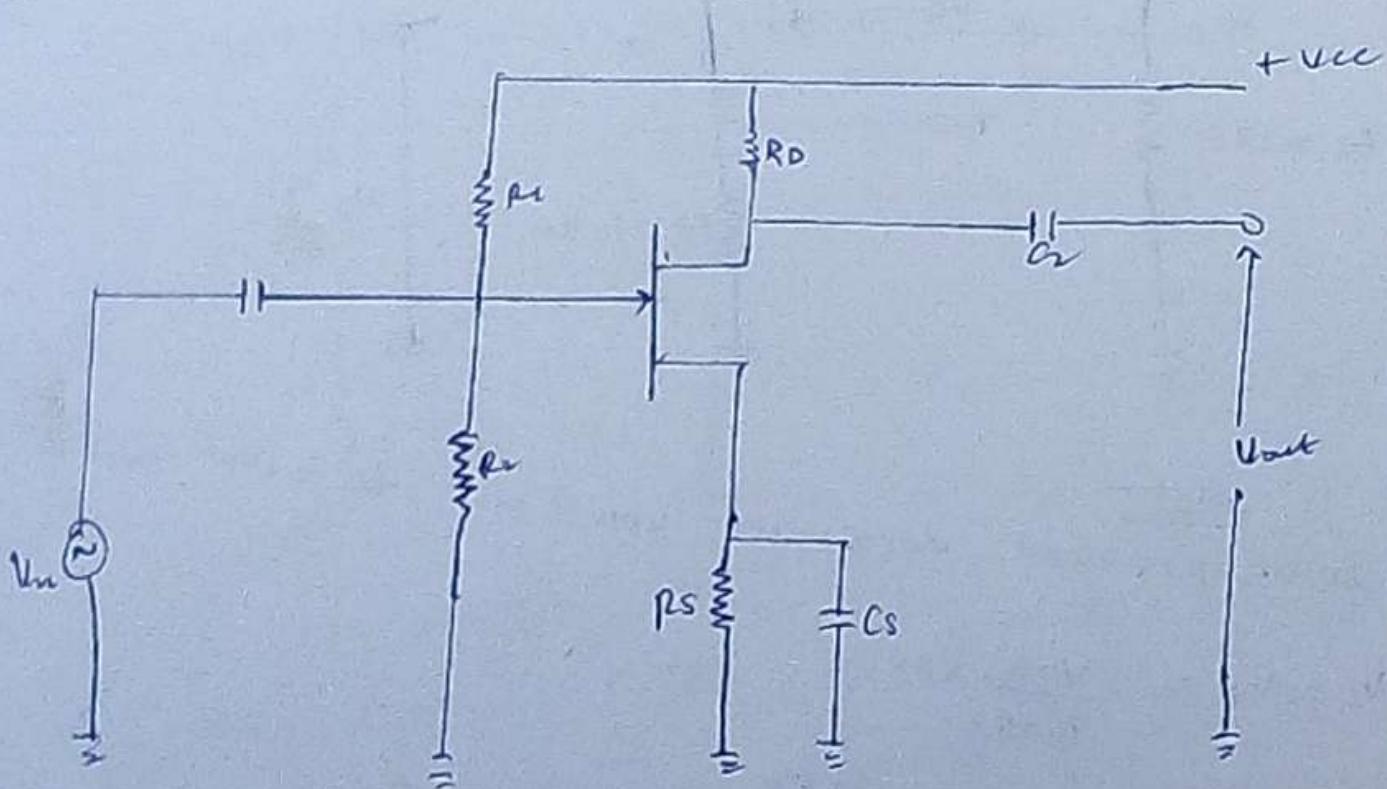

66

For the JFET of fig Q5 the Transconductance at zero gate to source voltage  $g_{m0} = 5 \text{ ms}$ . Determine the amplifier input resistance ( $R_s$ ) and a.c voltage gain ( $A_v = V_o/V_i$ ) assume the capacitors to be small.

Short circuit for  $v_o$

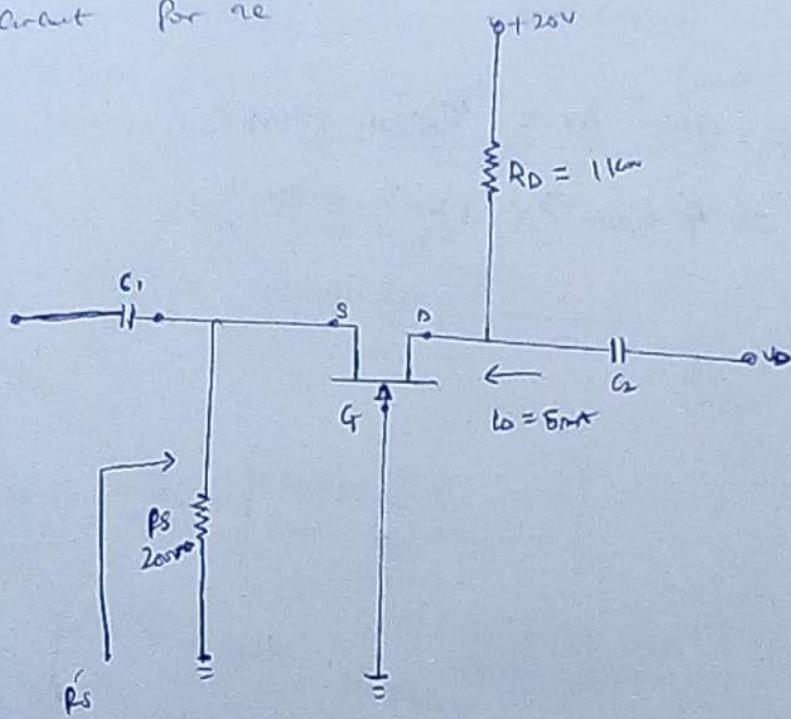

Solution

$$V_{DD} = 20V, I_D = 5\text{mA}, R_D = 1\text{k}\Omega \quad R_s = 200\Omega, g_{m0} = 5\text{ms}$$

Drain resistance  $r_d = \frac{V_{DS}}{I_D}$

$$g_m = g_{m0} \left[ 1 - \frac{v_{GS}}{V_{GS0}} \right]$$

$$V_{GS} = -I_D R_S = -(5\text{mA} \times 200) = -1V$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S) = 20 - 5\text{mA}(1000 + 200) \\ = 20 - 6 = 14V$$

$$V_F = V_{DS} = 14V$$

$$V_{GS(\text{eff})} = -14V$$

$$g_m = g_{m0} \left[ 1 - \frac{V_{GS}}{V_{GS(\text{eff})}} \right] = 5 \times 10^{-3} \left[ 1 - \frac{1}{-14} \right]$$

$$g_m = 5 \times 10^{-3} \left[ 1 - \frac{1}{14} \right], g_m = 5 \times 10^{-3} [0.9286] = 4.6 \text{ mS}$$

$$\text{Input resistance} = R_S \parallel \frac{1}{G_m} = 200 \parallel \frac{1}{4.6 \text{ ms}} \\ = 200 \parallel 215.39$$

$$R_D = \frac{200 \times 215.39}{200 + 215.39} = 63.7 \text{ } \cancel{\Omega}$$

AC voltage gain  $A_V = G_m R_D$


$$A_V = 4.6 \times 10^{-3} \times 1 \times 10^3 = 4.6 \text{ } \cancel{\Omega}$$

### Question 7

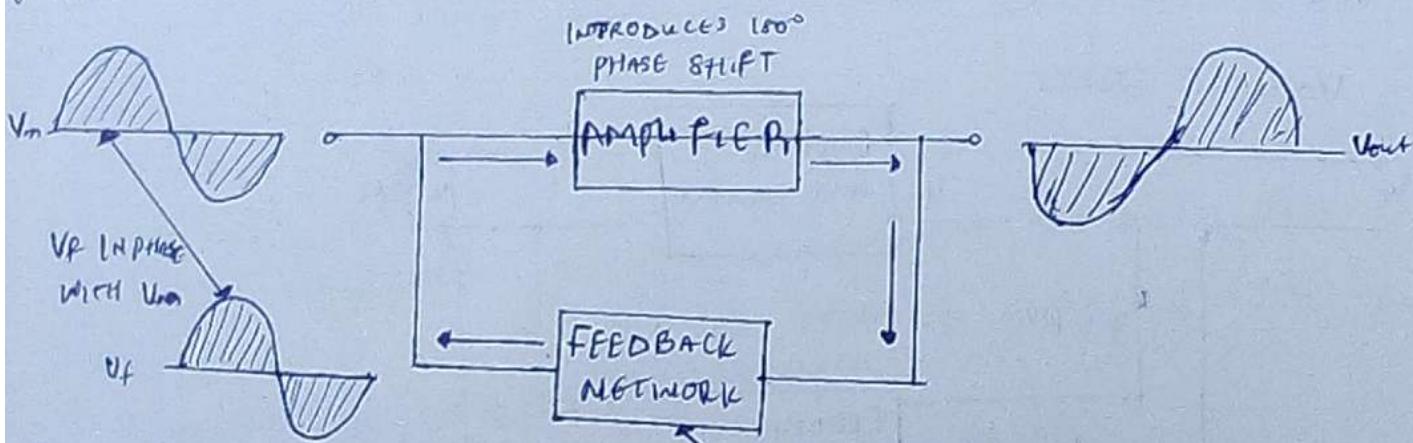- (a) Distinguish between positive and negative feedback amplifiers.

Answer


**POSITIVE FEEDBACK:** When the feedback energy (voltage or current) is in phase with the input signal and thus aids it, it is called positive feedback.



In the above illustration, both amplifier and feedback network introduce a phase shift of  $180^\circ$ . The result is  $360^\circ$  phase shift around the loop, causing the feedback voltage  $V_f$  to be in phase with the input signal  $V_i$ .

The positive feedback increases the gain of the amplifier. However, it has the disadvantages of increased distortion and instability. One important use of positive feedback is in oscillators.

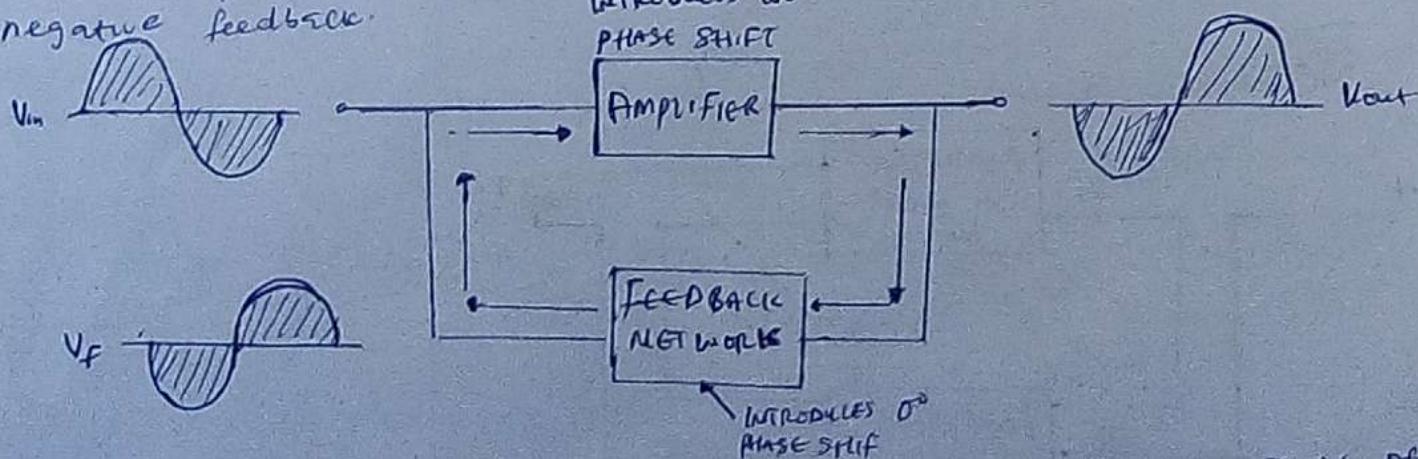**NEGATIVE FEEDBACK:** When the feedback energy (voltage or current) is out of phase with the input signal and thus oppose it, it is called negative feedback.



From the illustration above, the amplifier introduces a phase shift of  $180^\circ$  into the circuit while the feedback network is so designed that it introduces no phase shift (i.e.  $0^\circ$  phase shift). The result is that the feedback voltage  $V_f$  is  $180^\circ$  out of phase with the input signal.


Negative feedback reduces the gain of the amplifier. However, the advantages of negative feedback are: reduction in distortion, stability in gain, increased bandwidth and improved input and output impedance.

(7b)


Draw the block diagram of the following feedback networks.

- ① Voltage series ② Voltage shunt ③ Current series and ④ Current shunt


VOLTAGE SERIES

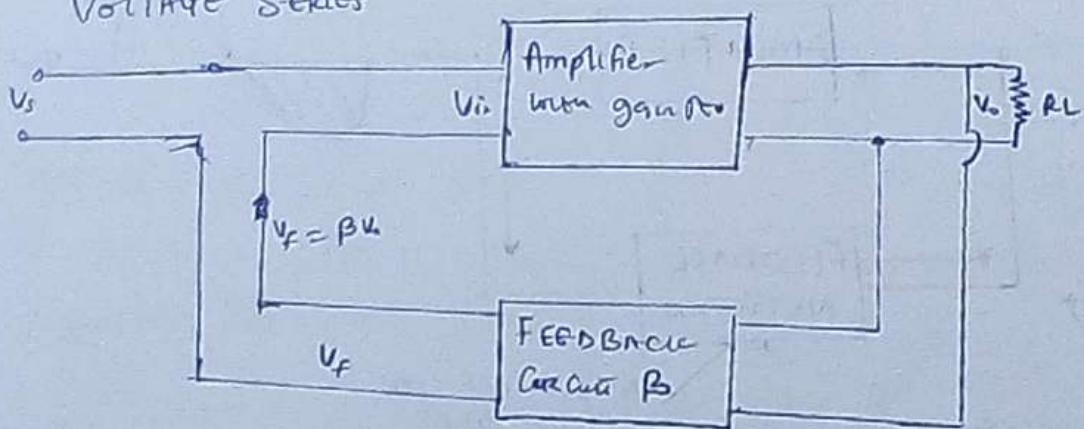


VOLTAGE SHUNT

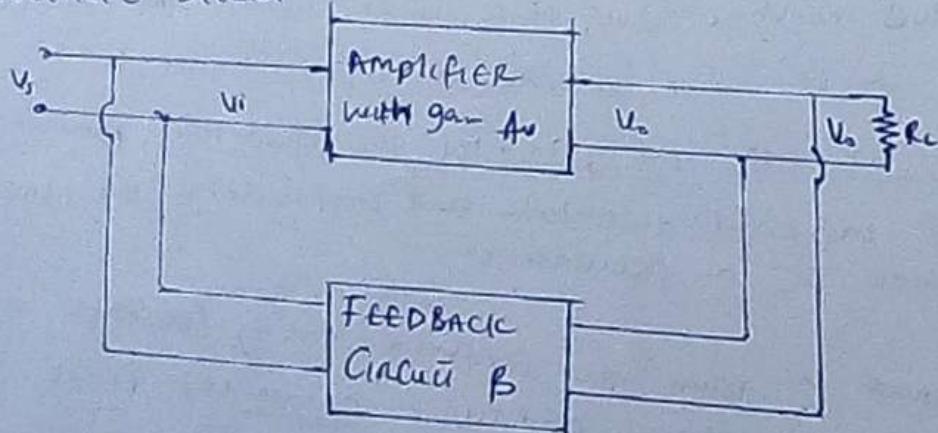

CURRENT SERIES

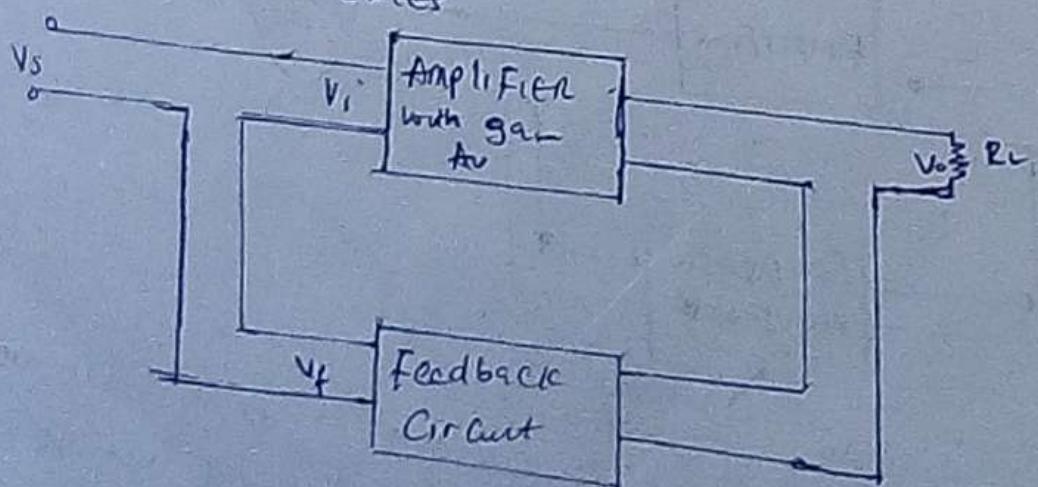


CURRENT - SHUNT FEEDBACK

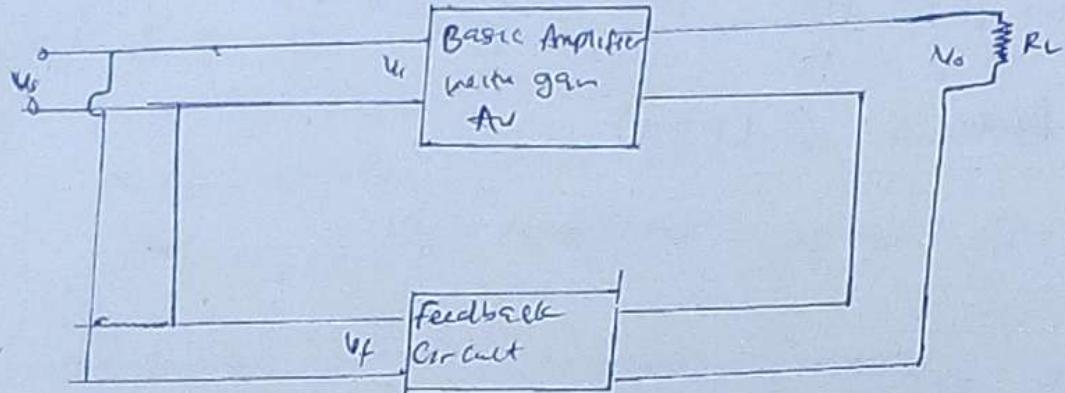

(7c)

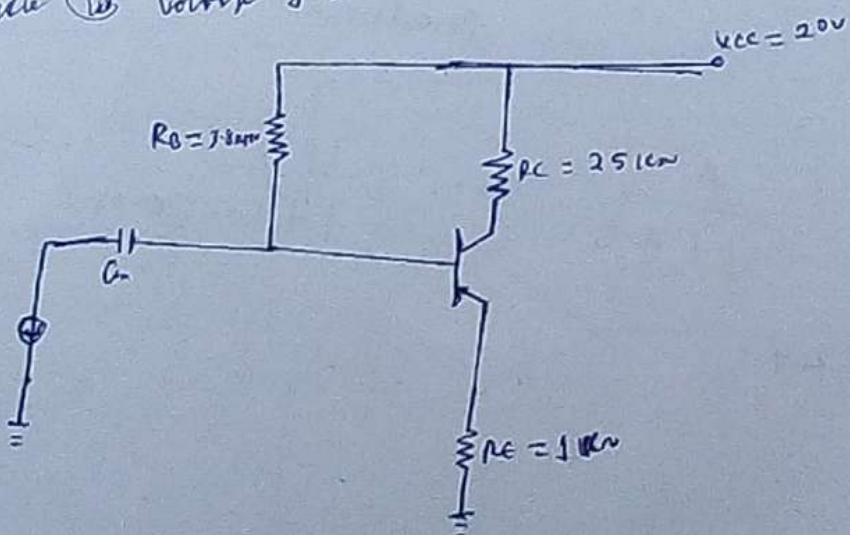- For the feedback amplifier circuit of fig below find  
 ④ feedback ratio ⑤ feedback factor ⑥ voltage gain without  
 feedback ⑦ voltage gain with feedback



Solution

$$V_{CC} = 20V \quad R_B = 3.8M\Omega \quad R_C = 25k\Omega \quad R_E = 1k\Omega \quad \beta = 100$$

Apply i-v law at collector side

$$\beta I_E = \frac{V_{CC}}{R_E + R_C} = \frac{20}{\left(\frac{3.8 \times 10^6}{200}\right) + (1 \times 10^3)} = \frac{20}{19000 + 1000} = \frac{20}{20000}$$

$$I_E = \frac{20}{20000} = 1mA$$

$$R_E = \frac{25mV}{I_E} = \frac{25mV}{1mA} = 25\Omega$$

$$\textcircled{L} \quad \text{feedback ratio } B = \frac{R_F}{R_C} = \frac{11k\Omega}{25k} = \frac{1}{2.5} = 0.04$$

$$\textcircled{V} \quad \text{The feedback factor} = (1 + BA)$$

where  $A$  is voltage with feed back

$$Av = \frac{R_C}{r_e} = \frac{25k\Omega}{25} = 1000$$

$$\text{Feedback factor} = (1 + BA) = 1 + 0.04(1000) = 41$$

$$\textcircled{m} \quad \text{Voltage gain without feedback}$$

$$Av = \frac{R_C}{r_e} = \frac{25k\Omega}{25} = 1000$$

$$\textcircled{w} \quad \text{Voltage gain with feedback}$$


$$A_{HF} = \frac{Av}{1 + AvB} = \frac{1000}{1 + 1000(0.04)} = \frac{1000}{41} = \underline{\underline{24.39}}$$

$$A_{HF} = 24$$


### Question 8

(A) Draw the circuit diagram of how an operational Amplifier can be configured as  
 ① 4 input summer ② Non Inverting Amplifier ③ Comparator  
 Analog Amplifier ④ Differential AMPLIFIER


① 4 Input summer

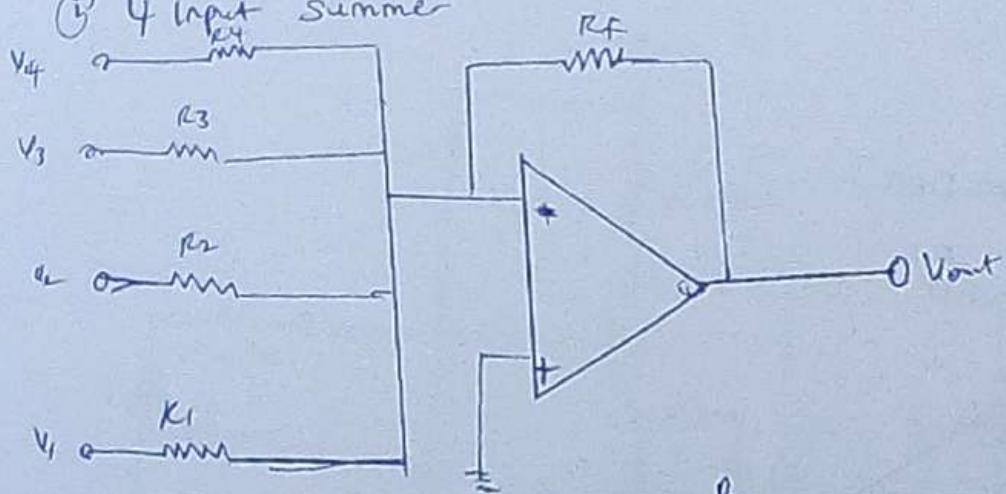


② Analog Amplifier

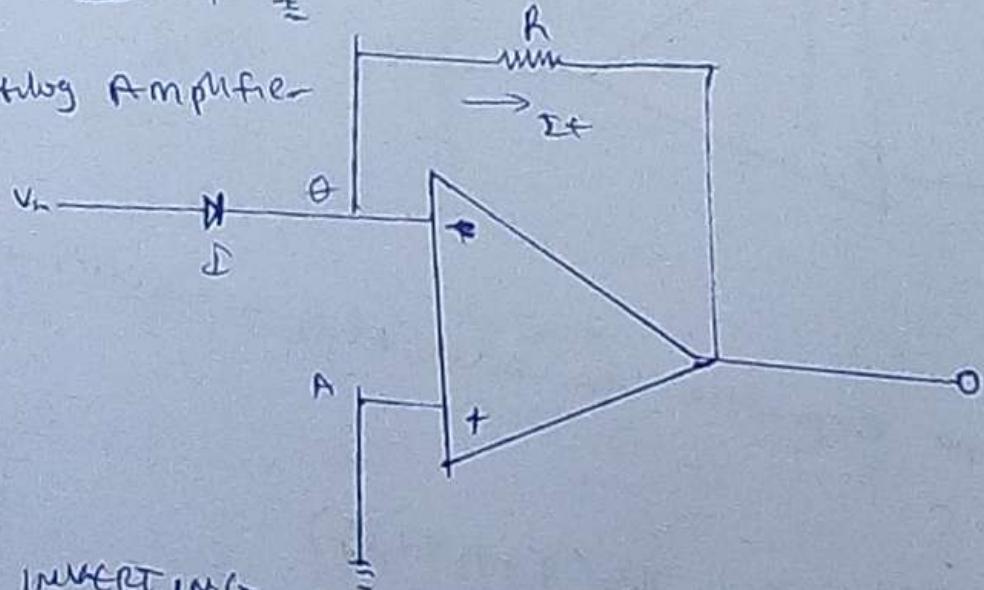


③ Non INVERTING

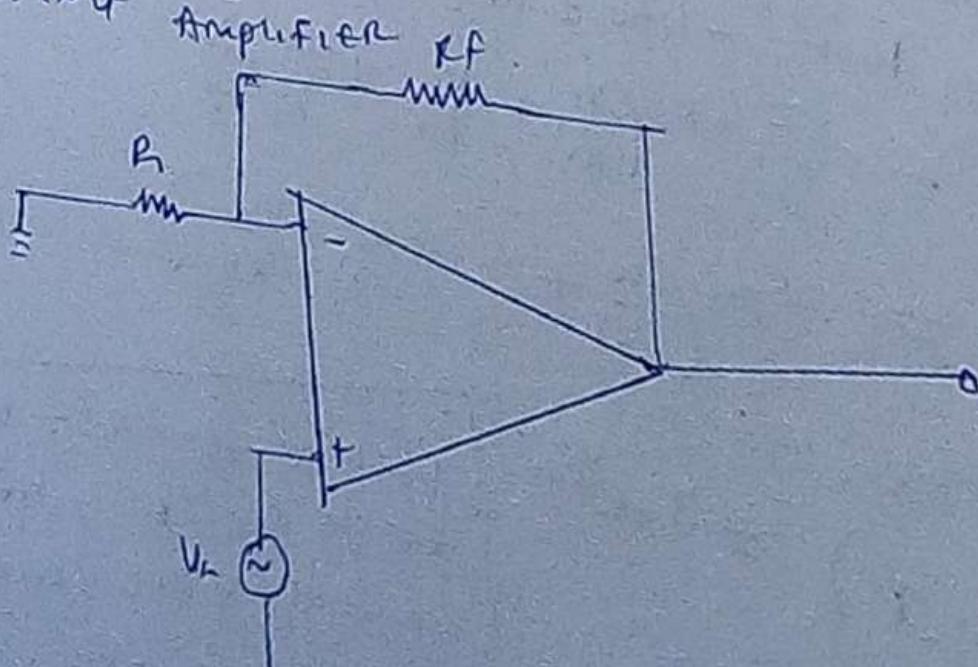

(W) COMPARATOR

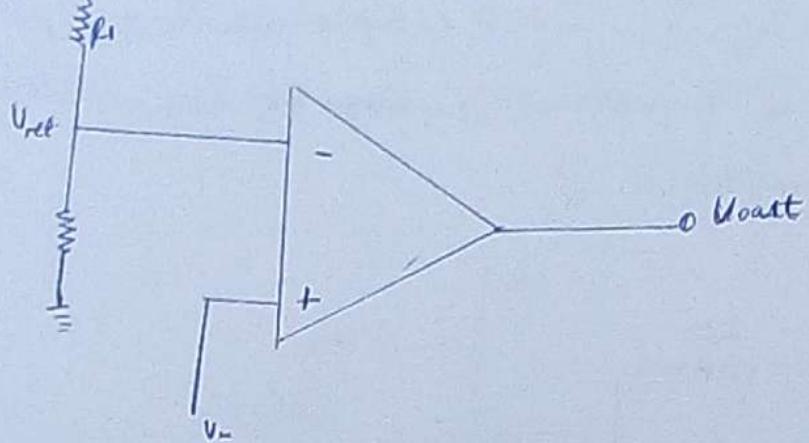

(Y) DIFFERENTIAL AMPLIFIER

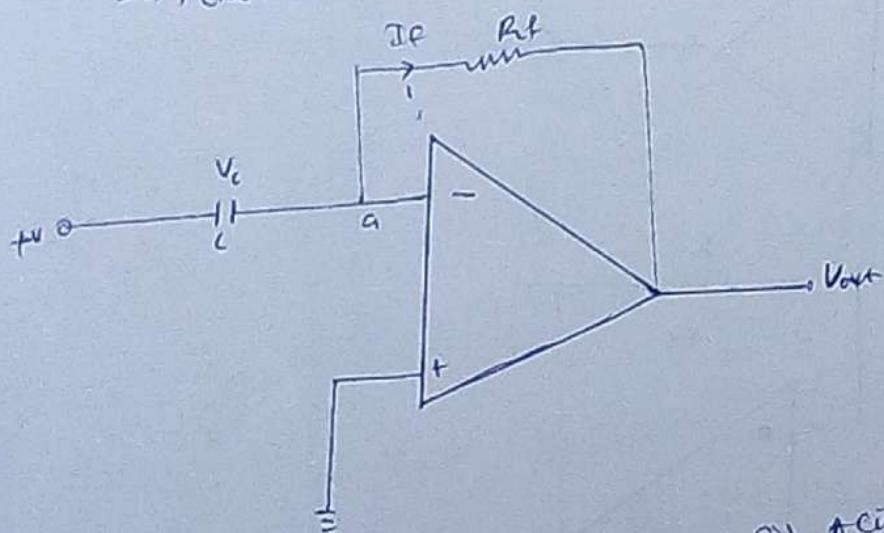

(B) Derive the output expression for  $A(A)$ ,  $A(C)$  and  $A(AC)$  above

(1) 4 input summer

$$\text{Output Voltage } V_{\text{out}} = -IAF = R_f (I_1 + I_2 + I_3 + I_4)$$

$$= -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_4}{R_4} \right)$$

$$V_{\text{out}} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_4}{R_4} \right)$$

(ii) Anti log Amplifier

$$I = I_0 \left( \frac{V_o}{P_m V_L} - 1 \right) \approx I_0 \frac{V_o}{P_m V_L}$$

$$V_o = V_m, V_{\text{out}} = -IA \cdot R_f$$

$$V_{\text{out}} = -R_f I_0 \frac{V_m}{P_m V_L}$$

$$\text{Voltage across } R_1 = V_m - 0$$

$$\text{Voltage across } R_f = V_{\text{out}} - V_m$$

Current through  $R_1$  = Current through  $R_f$


$$\frac{V_m - 0}{R_1} = \frac{V_{\text{out}} - V_m}{R_f}$$

(iii) Non Invertible:


$$\begin{aligned} V_m - V_o &= V_{\text{out}} R_1 - V_m R_f \\ \frac{V_o}{V_m} &= \frac{R_f + R_1}{R_1} = 1 + \frac{R_f}{R_1}, V_{\text{out}} = V_m \left( 1 + \frac{R_f}{R_1} \right) \end{aligned}$$

Question 9

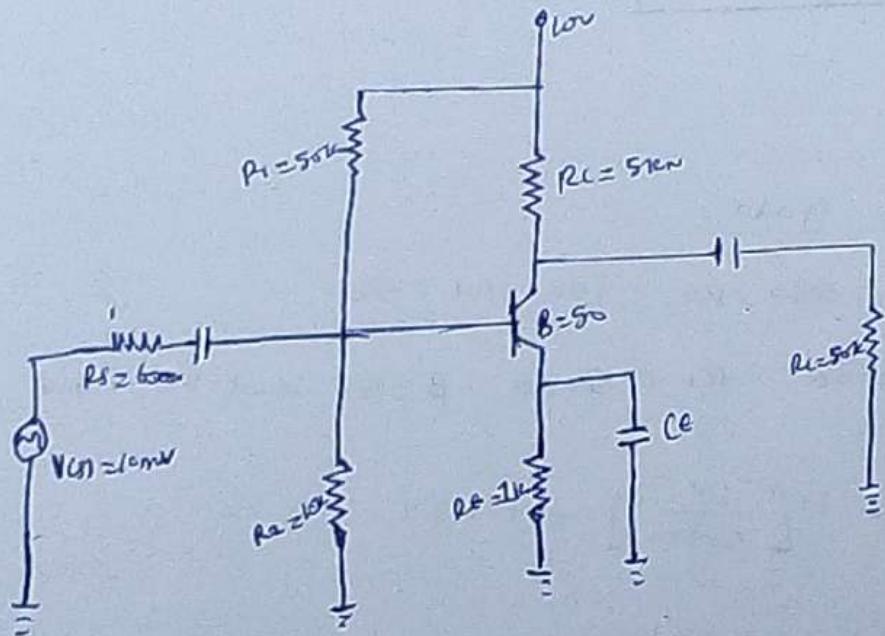
- (A) For the single stage amplifier shown in fig Q9, draw the DC and AC equivalent circuit
- (B) From the equivalent circuit of fig Q9, calculate the output voltage gain  $\text{u}$   $\leftarrow$  The overall voltage gain (since  $V_{BE} = 0.2V$ )



(A) DC equivalent circuit

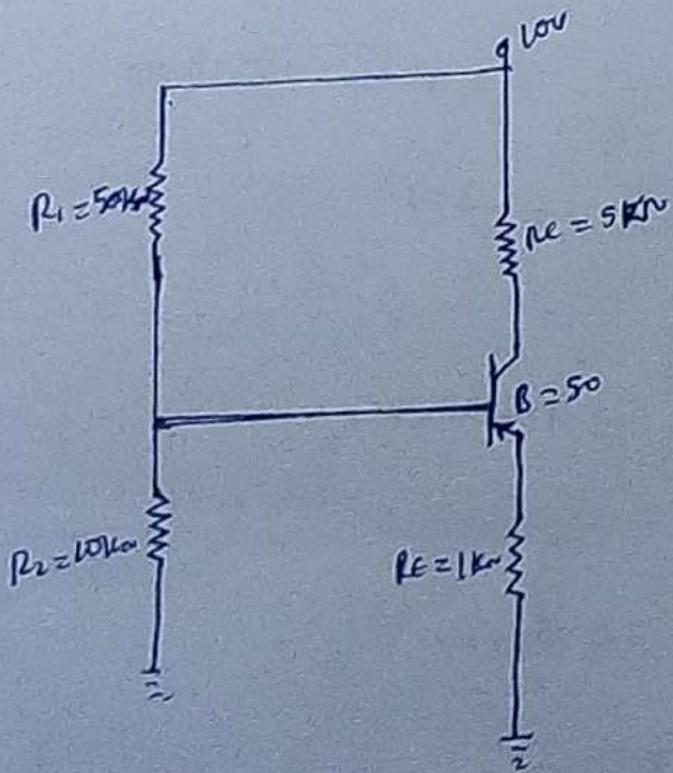

Question 9

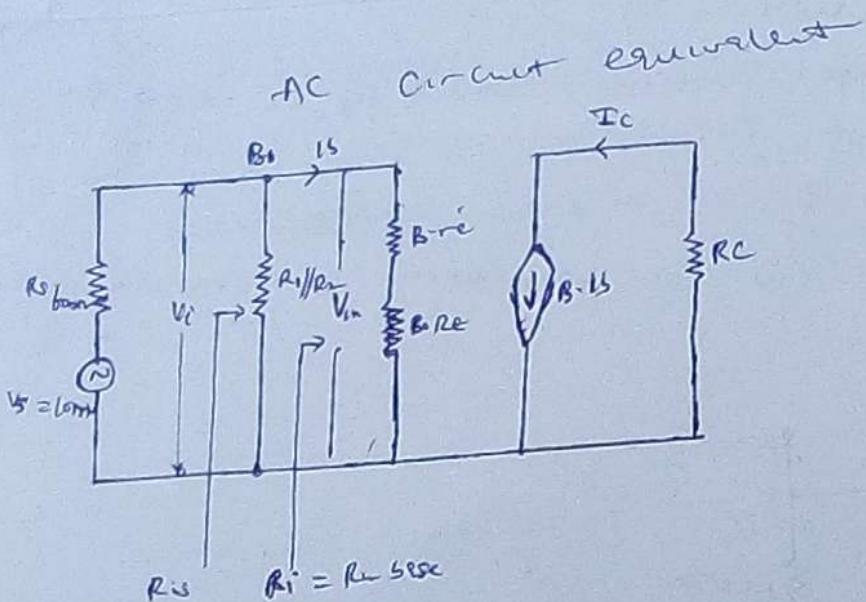

(A) Output voltage gain

Given  $V_{CC} = 10\text{V}$ ,  $R_C = 5\text{k}\Omega$ ,  $R_E = 1\text{k}\Omega$ ,  $R_L = 50\text{k}\Omega$

$R_2 = 10\text{k}\Omega$      $R_S = 6\text{k}\Omega$      $R_E = 50\text{k}\Omega$      $\beta = 50$  and  $V_s = 10\text{mV}$

Solution

$$V_{th} = V_{CC} \left[ \frac{R_2}{R_1 + R_2} \right] = 10 \left[ \frac{10}{50 + 10} \right] = 1.67\text{V}$$

$$R_{th} = R_1 // R_2 = \frac{(R_1 R_2)}{R_1 + R_2} = \frac{50 \times 10}{50 + 10} = 8.3\text{k}\Omega$$

$$I_E = \frac{V_{th} - V_{BE}}{R_E + R_{th}} = \frac{1.67 - 0.7}{1000 + 8.3 \times 10^3} = 0.83\text{mA}$$

$$\text{AC emitter resistance } r_e = \frac{25}{I_E} = \frac{25}{0.83} = 30\text{m}\Omega \approx 30\Omega$$

$$R_{in} = (R_{th} R_2) // (B \cdot r_e) = R_{th} // B \cdot r_e = \cancel{8.3}$$

$$B \cdot r_e = 50 \times 30 = 1500\text{m}\Omega = 1.5\text{k}\Omega$$

$$R_{in} = \cancel{\frac{8.3 \times 1.5}{8.3 + 1.5}} = R_{in} = \frac{8.3 \times 1.5}{8.3 + 1.5} = 1.27\text{k}\Omega$$

$$R_L = R_C // R_E = 5 // 50 = \frac{5 \times 50}{5 + 50} = 4.545\text{k}\Omega$$

$$AV = \frac{r_L}{r_e} = \frac{4.545 \times 10^3}{30} = 151.5$$

$$V_o = V_s \left[ \frac{R_{in}}{R_{in} + R_E} \right] = 10 \left[ \frac{1.27}{1.27 + 60} \right] = 6.79\text{mV}$$

Question 9


(b)  $V_o = A_v \times V_m = 151.5 \times 6.79 = 1.029^v$

overall voltage gain

$$A_{ov} = A_v \times \frac{V_m}{V_s} = 151.5 \times \frac{6.79}{10} = 102.9$$

Question 10

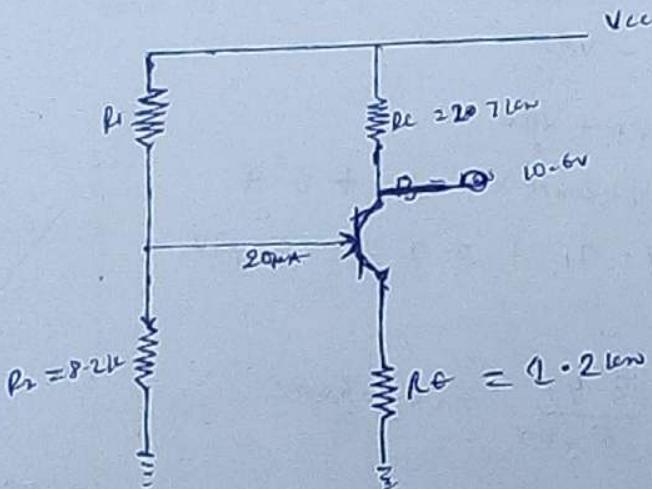(A) Calculate the following for the voltage divider configuration shown in fig below  
 i)  $I_C$  ii)  $V_E$  iii)  $V_{CE}$  iv)  $R_S$



Solution

$$V_{CC} = 12V, V_C = 10.6V, R_C = 2.7k\Omega, R_B = 20k\Omega$$

$$\text{Q) } I_C = V_C / R_C, I_C = \frac{10.6}{2.7k\Omega} = 3.926mA$$

$$I_C \approx I_E = 3.926mA$$

$$\text{W) } V_E = I_E R_E = 3.926mA \times 1.2k\Omega = 4.71V$$

(W)  $V_{CE}$   
 Applying K voltage down to collector side

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$V_{CE} = 12V - 3.926mA (2.7k\Omega + 1.2k\Omega) = 5.29V$$

$$V_{CE} = V_{CE} + I_C (R_C + R_E)$$

$$= 5.29 + 3.926mA (2.7k\Omega + 1.2k\Omega)$$

$$= 5.29 + 7.826 = 13.116V \approx 13V$$

$$V_{CE} = 13V$$

$$\textcircled{1} \quad \textcircled{iv} \quad U_{CE} = V_C - V_E = 10.6 - 4.71 = 5.29 \text{ V}$$

\textcircled{v} \quad R\_1

$$\text{Emitter Current } I_E = \frac{V_2 - V_{BE}}{R_E}$$

$$V_{BE} = V_2 - V_{BE}$$

$$\begin{aligned} V_B &= I_E + V_{BE} \\ &= (\beta \cdot 92 \text{ mA} \times 1.2 \text{ k}\Omega) + 0.7 \\ &= 4.71 + 0.7 = 5.41 \text{ V} \end{aligned}$$

$$I_2 = \frac{V_2}{R_2} = \frac{5.41}{6.2 \text{ k}\Omega} = 0.66 \text{ mA}$$

$$I_1 = I_B + I_2 = 0.66 \text{ mA} + 20 \text{ nA} = \cancel{0.68 \text{ mA}}$$

Since  $I_2 \gg I_B$ ,  $I_B$  can be neglected  $I_1 = 0.66 \text{ mA}$

$$I_1 = \frac{V_{CC}}{R_1 + R_2} = \frac{13.12}{R_1 + 8.2 \text{ k}\Omega}$$

$$0.66 \text{ mA} (R_1 + 8.2 \text{ k}\Omega) = 13.12$$


$$R_1 = \frac{13.12 - 5.412}{0.66 \times 10^{-3}} = \frac{7.708}{0.66 \times 10^{-3}} = 11678.78 \text{ }\Omega$$

$$\underline{\underline{R_1 = 11.7 \text{ k}\Omega}}$$

B)

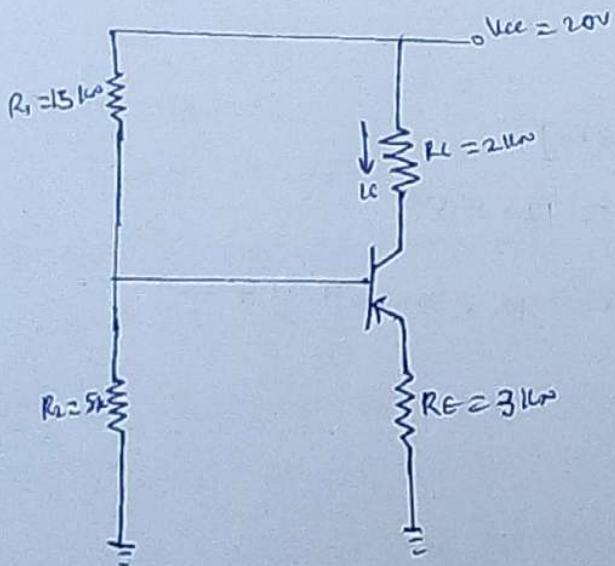Question 10

For the circuit in fig below, draw dc load line and mark the Q point of the Silicon transistor if  $V_{BE} = 0.7V$  and  $I_C = 4mA$ .



Solution

Given  $V_{BE} = 0.7V$   $V_{CC} = 20V$   $R_L = 2k\Omega$   $R_E = 3k\Omega$

D.C. load line

$$V_{CE} = -V_{CC} + I_C(R_C + R_E)$$

Negative sign of  $V_{CE}$  shown

reverse bias

$$V_{CE} = V_{CC} + I_C(R_C + R_E)$$

$I_{Cmax} = 4mA$  when  $V_{CE} = 0$

When  $I_C = 0$

$$V_{CE} = V_{CC} = 20V$$

Q point

Voltage across  $R_2$ ,  $v_2 = \frac{V_{CC}}{R_1 + R_2} \times R_2$


$$V_2 = \frac{20}{15+5} \times 5 = 5V$$

$$I_E = \frac{V_2 - V_{BE}}{R_E} = \frac{5 - 0.7}{3k\Omega} = 1.43mA$$

$$I_C \approx I_E = 1.43mA$$

$$\begin{aligned} V_{CE} &= V_{CC} - I_E(R_C + R_E) \\ &= 20 - 1.4mA [2k\Omega + 3k\Omega] \\ &= 20 - 1.4mA [5k\Omega] = 12.83V \end{aligned}$$

Operating point Q are 12.83V and 1.43mA

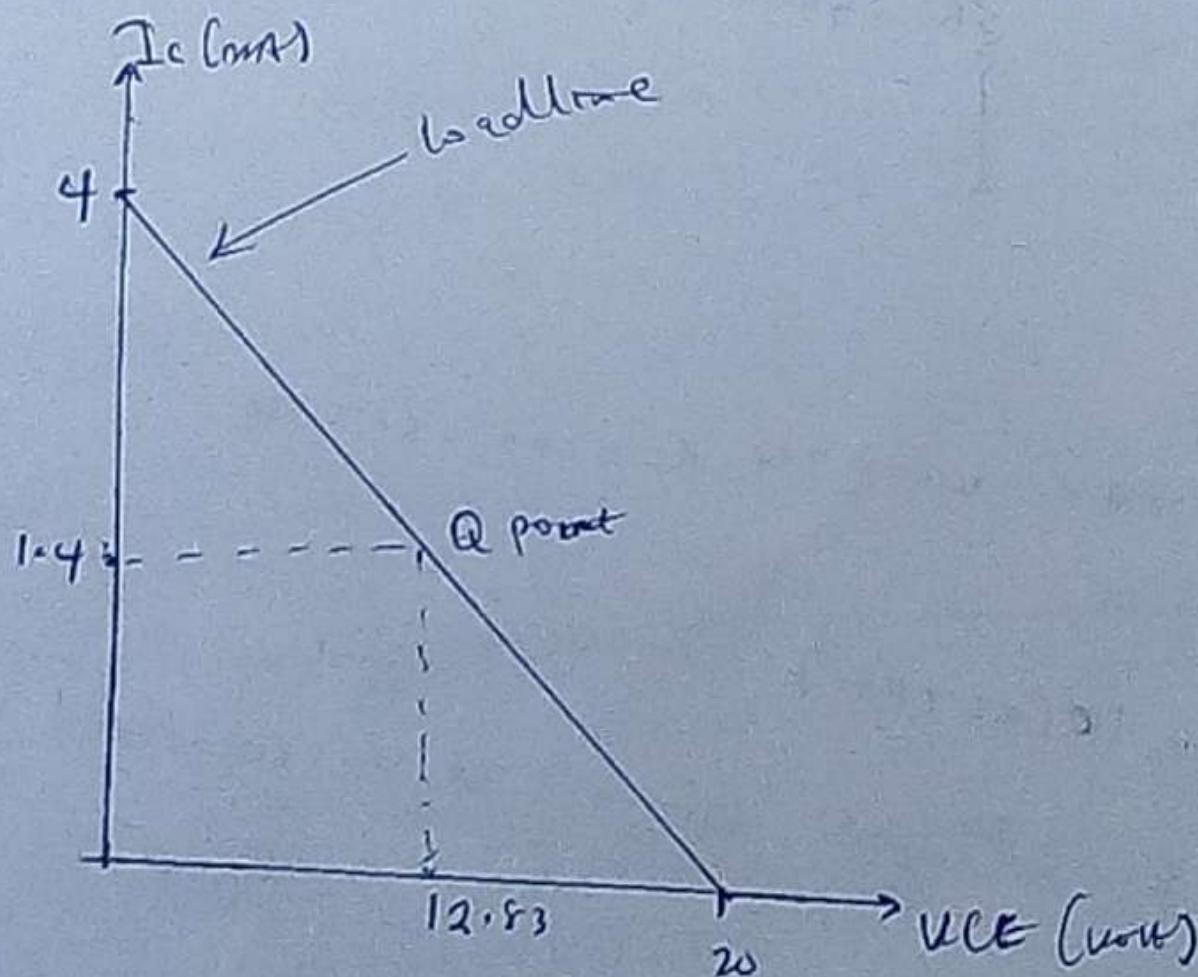

(13)


A List four characteristic of an ideal Op-Amp

### CHARACTERISTIC OF AN IDEAL OP-AMP

- ① The internal stages of an Op-Amp are direct-coupled i.e. no coupling capacitors are used. This coupling allows the Op-Amp to amplify dc as well as ac signals.
- ② An Op-Amp has very high input impedance (ideally infinite) and very low output impedance (ideally zero).
- ③ An Op-Amp has very high open-loop voltage gain (ideally infinite), typically more than 200,000.
- ④ Input stage of an Op-Amp is a differential amplifier (DA) and the output stage is typically a class B push-pull emitter follower.

(B)

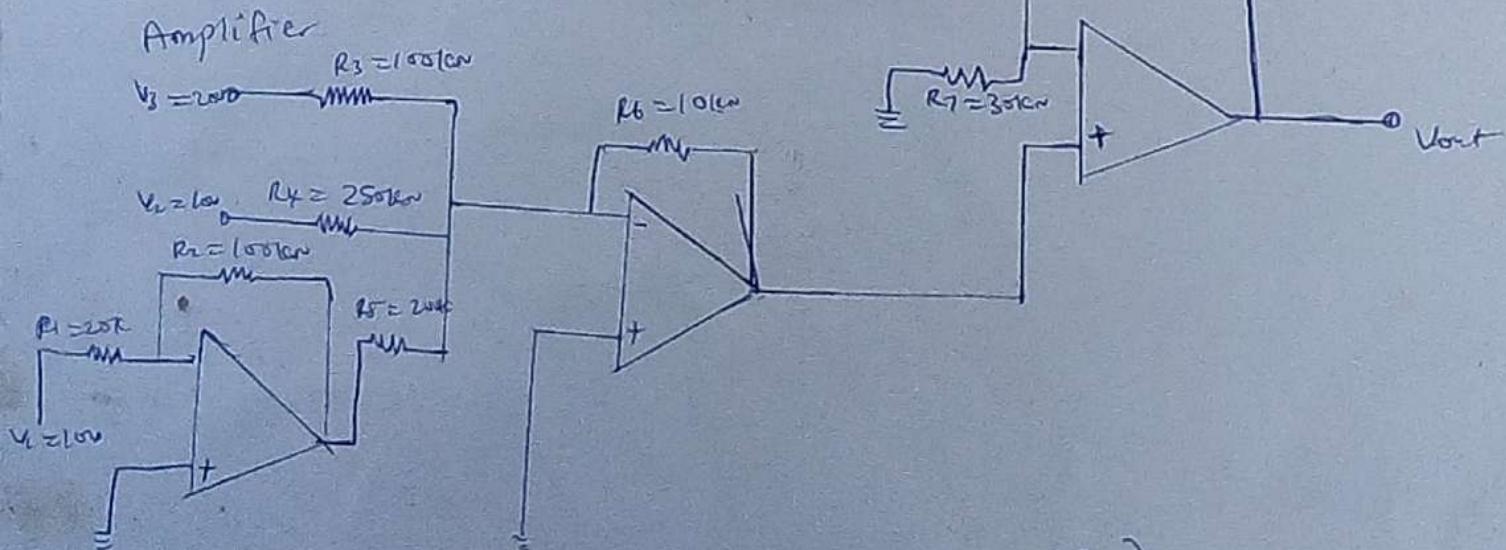Find the Output ~~Characteristics~~ of an ideal Op-Amp the multistage



$$V_{out} = -R_F \left[ \frac{V_1}{R_1} + \frac{V_2}{R_4} + \frac{V_3}{R_3} \right] \times -\frac{R_6}{R_5} \times \left( 1 + \frac{R_8}{R_7} \right)$$

$$V_{out} = -R_f \left[ \frac{V_1}{R_1} + \frac{V_2}{R_4} + \frac{V_3}{R_3} \right] x - \frac{R_6}{R_5} \times \left( 1 + \frac{R_f}{R_7} \right)$$

$$V_{out} = -R_2 \left[ \frac{V_1}{R_1} + \frac{V_2}{R_4} + \frac{V_3}{R_3} \right] x - \frac{R_6}{R_5} \times \left( 1 + \frac{R_f}{R_7} \right)$$

~~V<sub>out</sub>~~ ~~too~~  
Since all resistances are in ~~too~~ kΩ

$$= -100 \left[ \frac{10}{20} + \frac{10}{250} + \frac{20}{100} \right] x - \frac{10}{200} \times \left( 1 + \frac{60}{30} \right)$$

$$= -100 \left[ \frac{37}{500} \right] \times \left( -\frac{10}{20} \right) \times 3$$

$$V_{out} = 11.1 \text{ V}$$

14C

Given that the gain of an amplifier in a feedback arrangement is 10, the feedback factor  $B$  is 2, the input and output resistance is  $R_i = 25\Omega$  and  $R_o = 140$  respectively, calculate the feedback amplifier input resistance  $R_i'$  and output resistance  $R_o'$  for the four networks of question 7(b) above.

Solution

$$\text{Given } A_v = 10, B = 2 \quad R_i = 25\Omega \quad R_o = 140\Omega$$

(i) For voltage series

$$R_i' = (1 + B \cdot A_v) R_i$$

$$R_i' = (1 + 2 \cdot 10) \times 25 = 21 \times 25 = 525\Omega$$

$$R_o' = \frac{R_o}{1 + B \cdot A_v} = \frac{140}{1 + 2 \cdot 10} = \frac{140}{21} = 6.7\Omega$$

(ii) For voltage shunt

$$R_i' = \frac{R_i}{1 + B \cdot A_v} = \frac{25}{1 + 2 \cdot 10} = \frac{25}{21} = 1.19\Omega$$

$$R_o' = \frac{R_o}{1 + B \cdot A_v} = \frac{140}{21} = 6.7\Omega$$

(iii) For current shunt

$$R_i' = \frac{R_i}{1 + B \cdot A_v} = \frac{25}{21} = 1.19\Omega$$

$$R_o' = (1 + B \cdot A_v) R_o = (21) \times 140 = 2.94\text{k}\Omega$$

(iv) For current series

$$R_i' = (1 + B \cdot A_v) R_i = (1 + 20) 25 = 20 \times 25 = 525\Omega$$

$$R_o' = (1 + B \cdot A_v) R_o = 25 \times 140 = 2.94\text{k}\Omega$$