


\Rightarrow

Circuit

\Rightarrow Limitations of Ohm's law

\Rightarrow Kirchhoff's laws (1824 - 877)

① First law

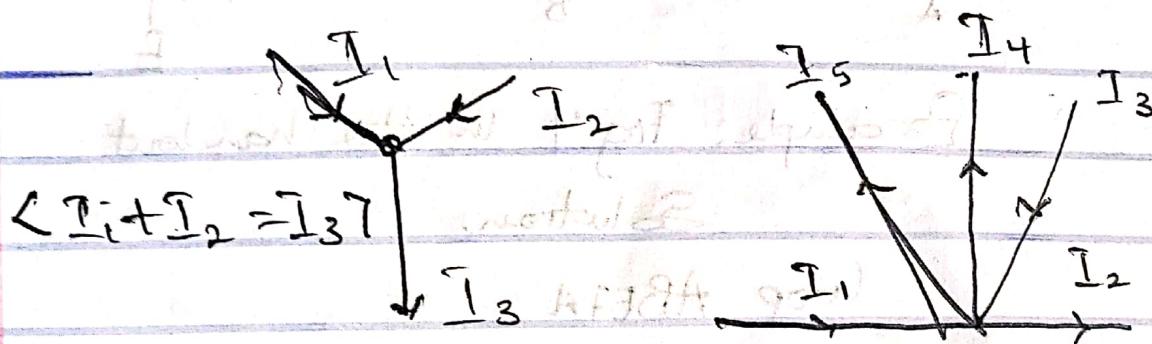


② Second law (Mesh or Voltage law)

Potential rise $\sum E = \sum IR$ - Potential voltage drops.


$$\sum E - \sum IR = 0$$

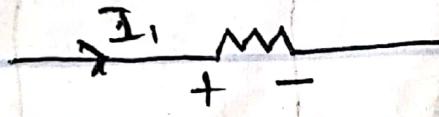
THE END OF A RESISTOR THROUGH WHICH CURRENT ENTERS, IS THEN POSITIVE, WITH RESPECT TO THE OTHER END



Rules Applied When Tracing Single Circuit

1) Voltage drop

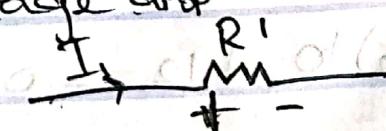

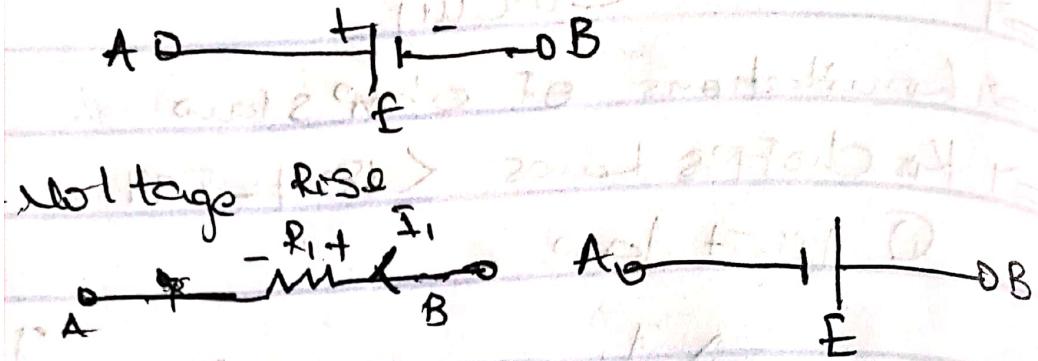

Example: Fig 4 in the handout.

Solution.

Loop ABFA

$$-I_1 R_1 - I_3 R_3 + E_1 = 0$$


$$E_1 = I_1 R_1 + I_3 R_3 \quad \text{--- (1)}$$

Loop BCDEFB

$$I_2 R_2 - E_2 + I_3 R_3 = 0$$

$$E_2 = I_2 R_2 + I_3 R_3 = E_2$$

Example 1.12 n

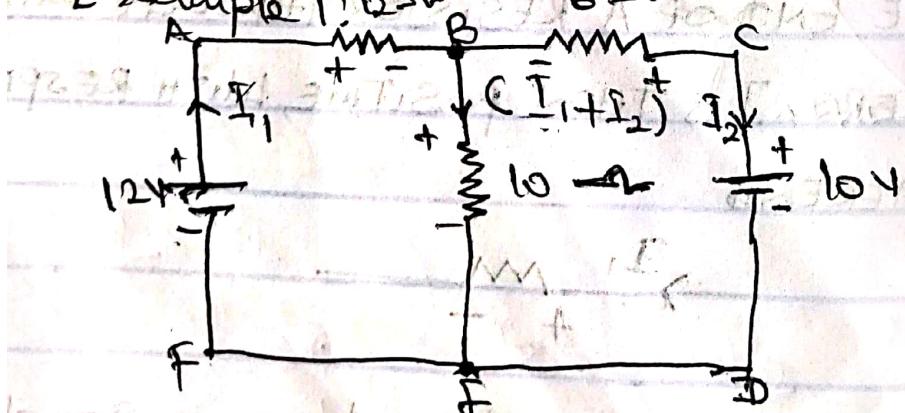

ABEF loop

$$-I_1 R_2 = (I_1 + I_2) 10 + 12 = 0$$

$$-I_{12} - I_1 10 + I_2 10 + I_2 = 0$$

$$-22I_1 + 6I_2 + I_2 = 0 \quad \text{--- (1)}$$

~~$$-22I_1 + 5I_2 - 6 = 0 \quad \text{--- (2)}$$~~

BCD loop

$$6I_2 - 10 + 6(I_1 + I_2) = 0$$

$$6I_2 - 10 + 10I_1 + 10I_2 = 0$$

~~$$16I_2 - 10 + 10I_1 = 0$$~~

~~$$10I_1 + 16I_2 - 10 = 0$$~~

~~$$5I_1 + 8I_2 - 5 = 0 \quad \text{--- (3)}$$~~

~~$$11I_1 + 5I_2 - 6 = 0 \quad \text{--- (4)} \times 5$$~~

~~$$5I_1 + 8I_2 - 5 = 0 \quad \text{--- (5)} \times 11$$~~

~~$$55I_1 + 25I_2 - 30 = 0$$~~

~~$$55I_1 + 88I_2 - 55 = 0$$~~

~~$$-63I_2 + 25 = 0$$~~

$$\frac{-63I_2}{-63} = \frac{-25}{-63}$$

$$I_2 = 0.3974$$

Substituting I_2 into equation 1.

$$11I_1 + 5(0.3974) - 6 = 0$$

$$11I_1 - 4.013 = 0$$

$$I_1 = \frac{4.03}{11} = 0.3648 \approx 0.365 \text{ A}$$

Hence, Current through 12Ω resistor, $I_1 = 0.365 \text{ A}$

Current through 6Ω Resistor, $I_2 = 0.397 \text{ A}$

Current through 10Ω Resistor, $I_1 + I_2 = 0.762 \text{ A}$


The Voltage drop across;

$$12\Omega \text{ Resistor} = 0.365 \times 12 = 4.38 \text{ V}$$

$$6\Omega \text{ Resistor} = 0.397 \times 6 = 2.38 \text{ V}$$

$$10\Omega \text{ Resistor} = 0.762 \times 10 = 7.62 \text{ V}$$

Example 10.150

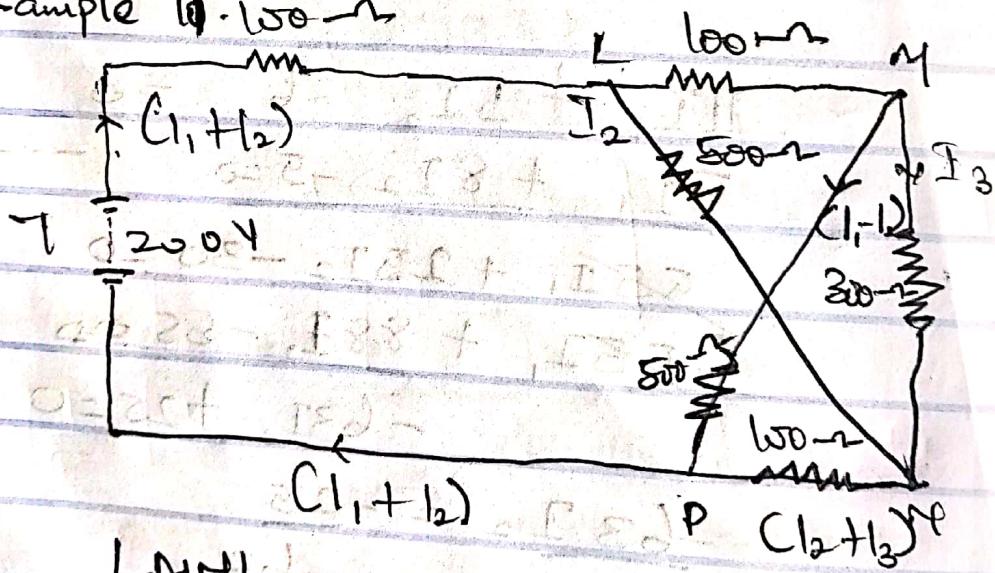

LNML


$$-100I_1 - 300I_2 + 500I_3 = 0$$

$$I_1 - 3I_3 + 5I_2 = 0$$

$$\text{Loop MNPM } \leftarrow -300I_3 - 100(I_2 + I_3) + 500(I_1 - I_3) = 0 \quad (1)$$

$$I_1 - 0.2I_2 + 1.8I_3 = 0$$

31/05/2023 Net Modal analysis.

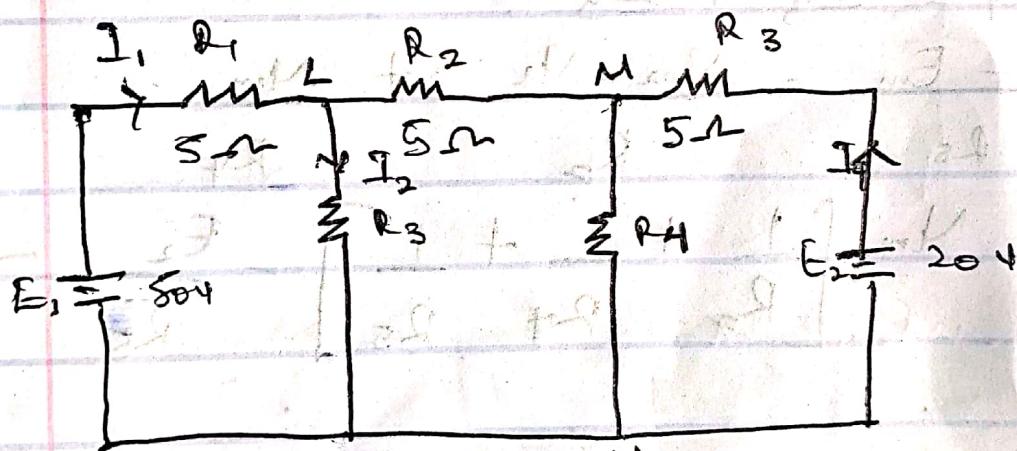

$$\text{No of equations} = n - 1 = 3 - 1 = 2$$

$$I_1 = I_2 + I_3$$

$$I_1 = E_1 - Ne$$

$$I_2 = \frac{Ne}{R_3}, \quad I_3 = \frac{Ne - E_2}{R_2}$$

$$\frac{E_1 - V_L}{R_1} + \frac{-V_L}{R_3}$$

$$\frac{V_L - V_m}{R_1} = \frac{V_L}{R_1} + \frac{V_L - V_m}{R_3}$$

$$\frac{V_L}{R_1} + \frac{V_L}{R_2} + \frac{V_L}{R_3} - \frac{E_1}{R_1} - \frac{V_m}{R_2}$$

$$\left\{ V_L \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{E_1}{R_1} - \frac{V_m}{R_2} \right\} = 0$$

$$I_4 = I_3 + I_5$$

$$\frac{E_1 - E_m}{R_5} = \frac{V_m - V_L}{R_2} + \frac{V_m}{R_4}$$

$$\frac{E_1 - V_m}{R_5} \left[\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_5} \right] - \frac{E_1}{R_5} - \frac{V_L}{R_2} = 0$$

$$V_L \left(\frac{1}{5} + \frac{1}{5} + \frac{1}{5} \right) - \frac{50}{3} - \frac{V_m}{5} = 0 \quad \dots \textcircled{1}$$

$$V_m \left(\frac{1}{5} + \frac{1}{5} + \frac{1}{5} \right) - \frac{20}{3} - \frac{V_L}{5} = 0 \quad \dots \textcircled{2}$$

$$\text{Equation 1} = 2.5V_L - V_m - 50 = 0$$

$$\text{Equation 2} = 2.5V_m - V_L - 20 = 0$$

$$V_L = 27.80$$



$$V_m = 19.05V$$

$$I_2 = \frac{V_L}{L} = \frac{27.6}{10} = 2.76 A$$

$$I_3 = \frac{V_m}{L} = \frac{19.05}{10} = 1.905 A$$

\Rightarrow Superposition Theorem

This theorem

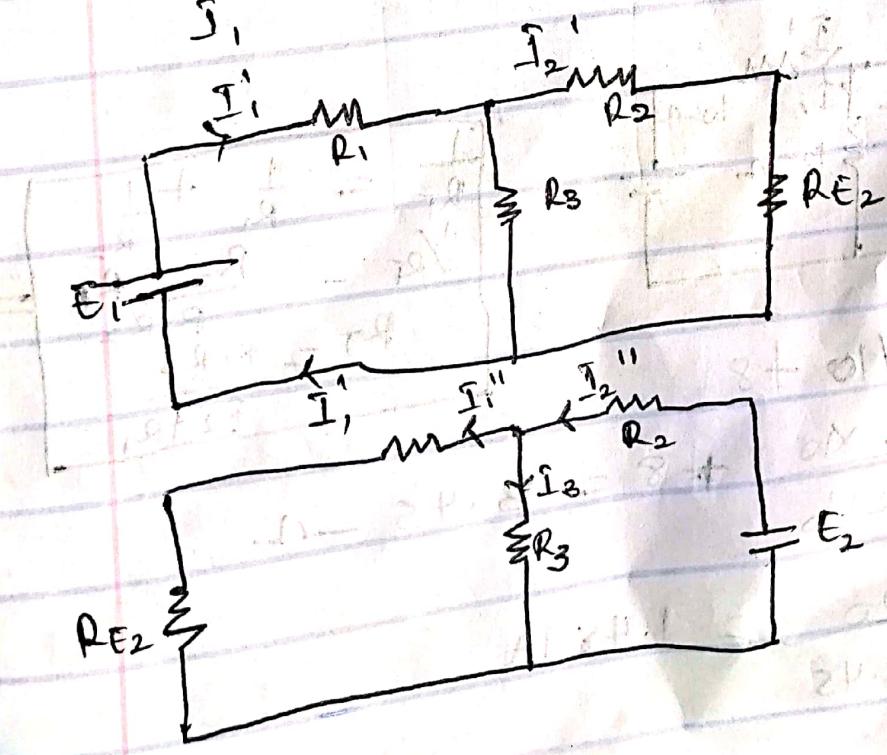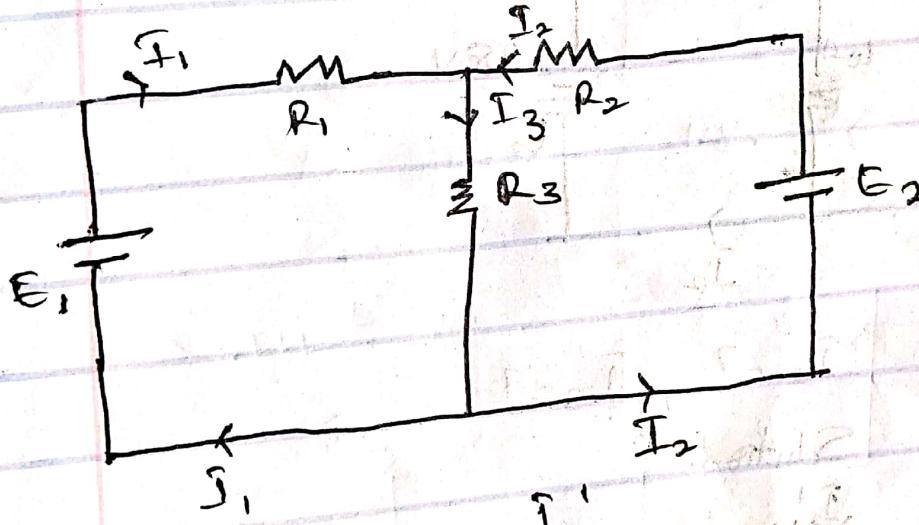


$$I_3 = I_3' + I_3''$$

$$I_1 = I_1' + I_1''$$


$$I_2 = I_2' + I_2''$$

$$I_2 = I_2'' - I_2'$$

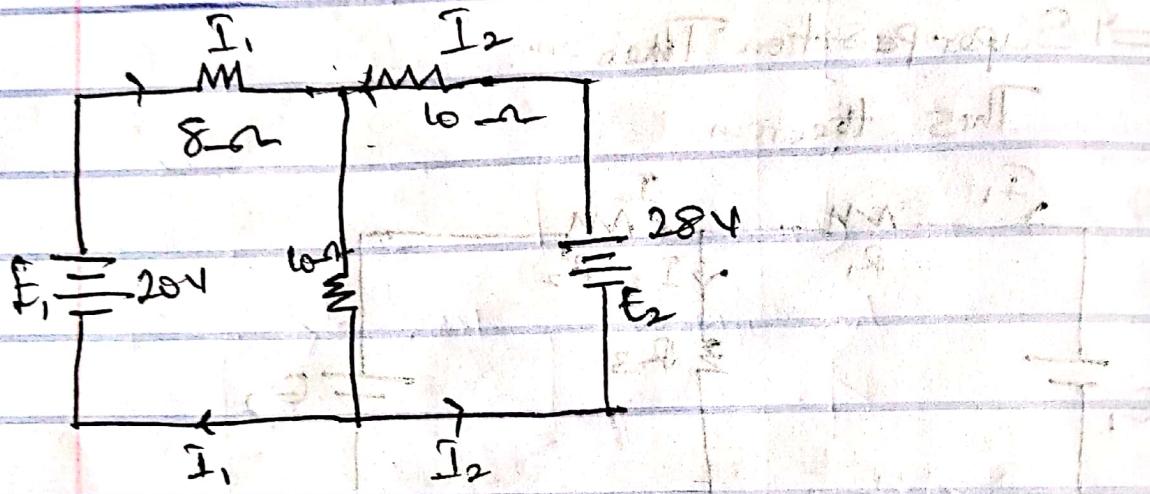

$$I_1 = ?, \quad I_2 = ?, \quad I_3 = ?$$

Solution

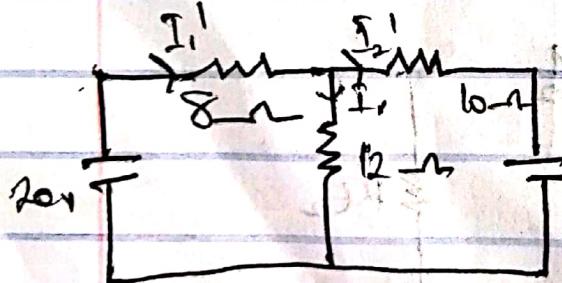

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{R_2 + R_1}{R_1 R_2}$$

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

NOTE

\parallel means
Parallel $R_T = 12 // 10 + 8$

$$R_T = \frac{12 \times 10}{12 + 10} + 8 = 13.45 \Omega$$


$$I = \frac{20}{13.45} = 1.489 A$$

$$\frac{I_1}{I_2} = 1.487 \times \frac{12}{10+12}$$

$$= 0.81 A$$

$$I_1' = 1.487 \times \frac{10}{10+12} = 0.675 A$$

CURRENT DIVIDER.

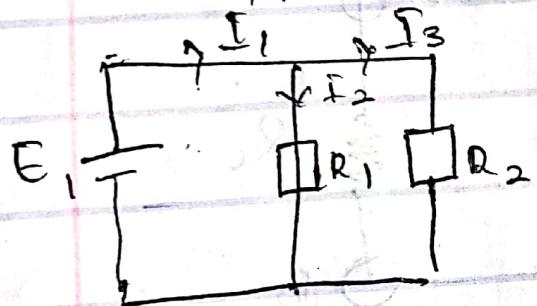

$$I_2 = I_1 \times \frac{R_2}{R_1 + R_2}$$


$$I_3 = I_1 \times \frac{R_1}{R_1 + R_2}$$

$$R_T = 6 + 12/8 = 14.8 \Omega$$

$$I_2'' = 28 / 14.8 = 1.892 A$$

$$I_1'' = 1.892 \times \frac{12}{12+8} = 1.135 A$$
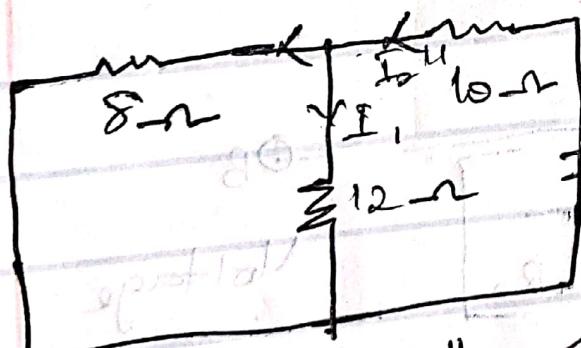
$$I_3'' = 1.892 \times \left(\frac{8}{12+8}\right) = 0.757 A$$



$$I_1 = I_1' - I_2'' = 6.352 A$$

$$I_2 = I_2'' - I_1' = 1.892 A - 0.81 = 1.082 A \text{ (from L to m)}$$

$$I_3 = I_1' + I_2'' = 0.675 + 0.757 = 1.432 A \text{ (from m to n)}$$


6/6/2023

Thevenin's

$$I = \frac{E_{th}}{R_{th} + R_L}$$
$$I = \frac{E}{R_1 + R_2}$$
$$E_{th} = I \times R_2$$
$$E_{th} = \frac{E}{R_1 + R_2} \times R_2$$

$$E_{th} = N_{oc}$$

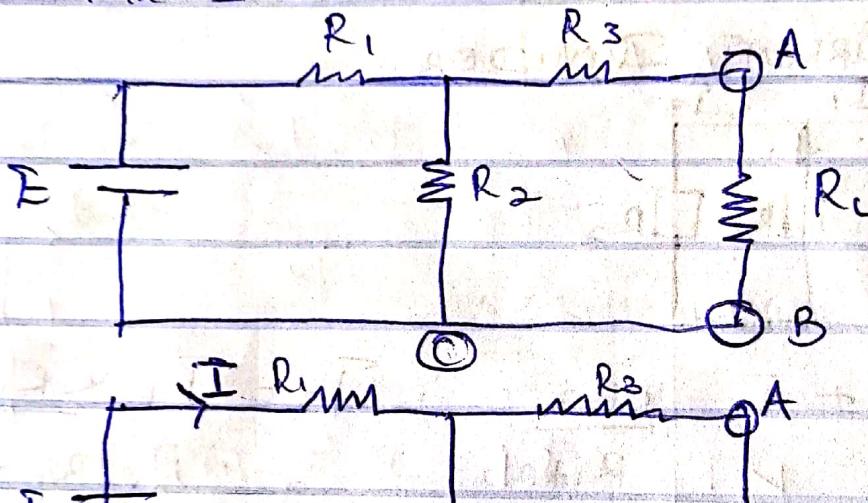R_{th} = Equivalent Resistance of the N_{th}



$$E_{th} = E \times \frac{R_2}{R_1 + R_2}$$


Voltage c

$$I = \frac{V}{R_{th}}$$


$$I = \frac{E}{R_1 + R_2}$$

$$E_{th} = I \times R_2 =$$
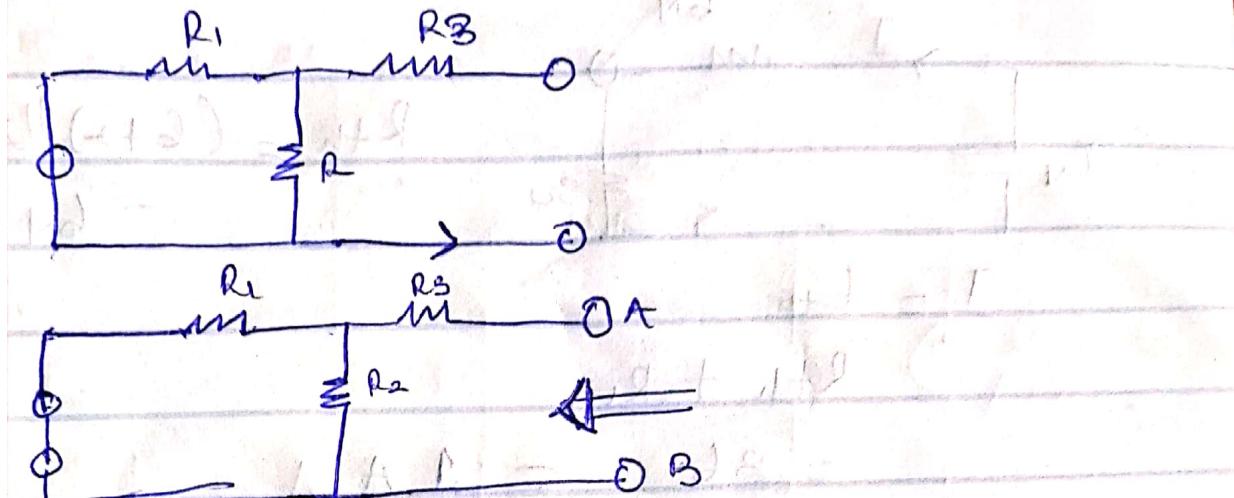
$$E_{th} = \frac{E}{R_1 + R_2} \times R_2$$




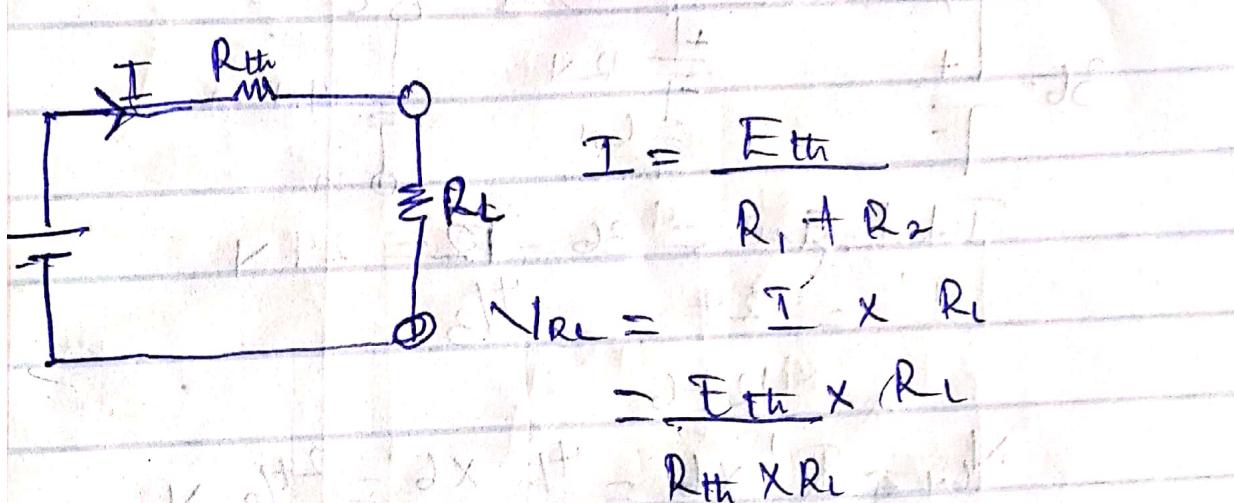
$$R_{th} = R_1 // R_2 + R_3 = \frac{R_1 R_2}{R_1 + R_2} + R_3$$




$$I = \frac{E_{th}}{R_1 + R_2}$$
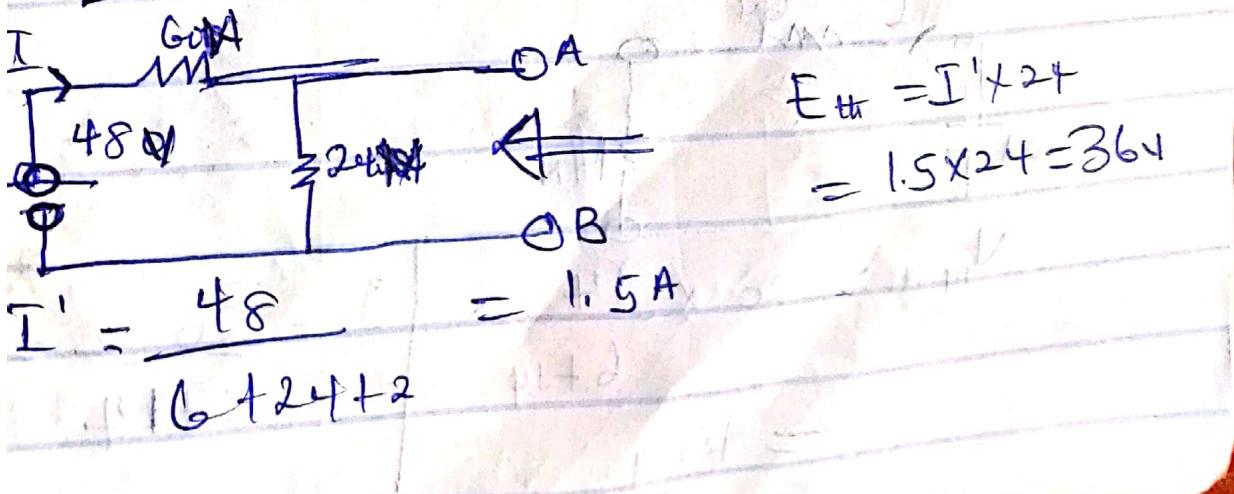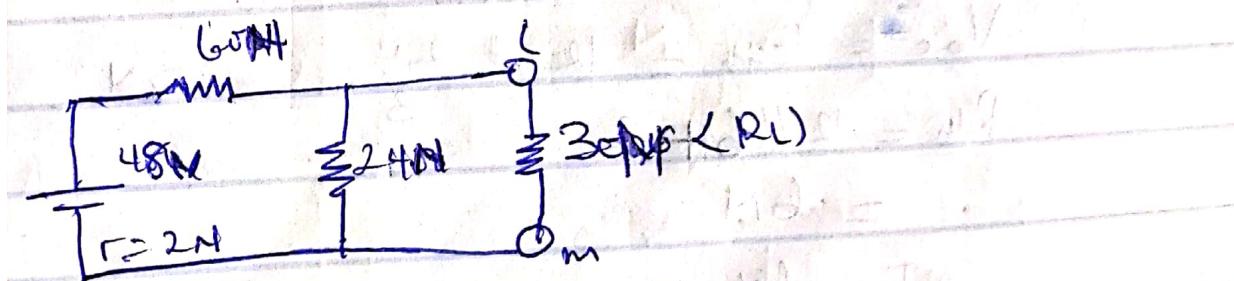
$$V_{RL} = \frac{I}{R_{th} + R_L} \times R_L \\ = \frac{E_{th} \times R_L}{R_{th} + R_L}$$



$$E_{th} = I' \times 24 \\ = 1.5 \times 24 = 36V$$

$$I' = \frac{48}{16 + 24 + 2} = 1.5A$$

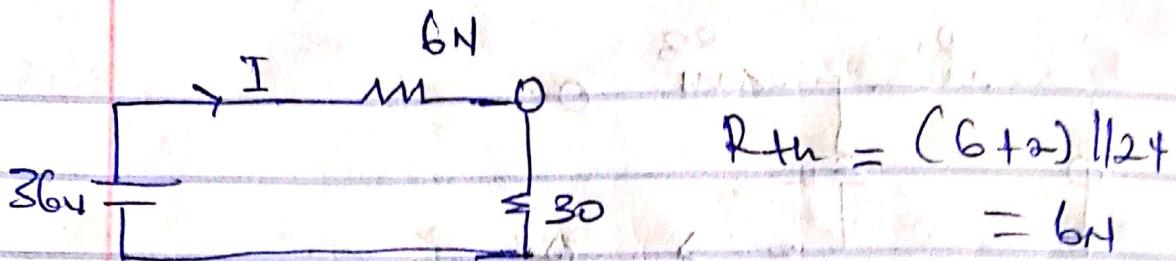


$$I = \frac{E_{th}}{R_{th} + R_L}$$

$$R_{th} + R_L >$$

$$= 36 \quad = 1A$$

$$6 + 30$$

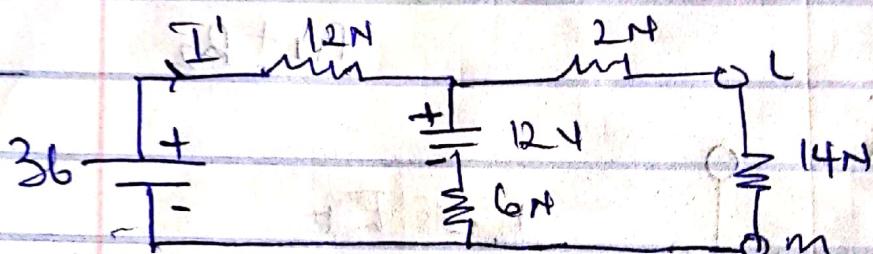

$$\text{Total } E_{th} = 36 - 12 = 24V$$


$$I' = \frac{24}{12+6} = \frac{4}{3}$$

$$V_{6N} = I' \times 6 = \frac{4}{3} \times 6 = 8V$$

$$V_{oc} = E_{th} = 12 + \frac{24}{3} = 20V$$

$$R_{th} = 12/12+6 = 2$$


$$= 6N$$

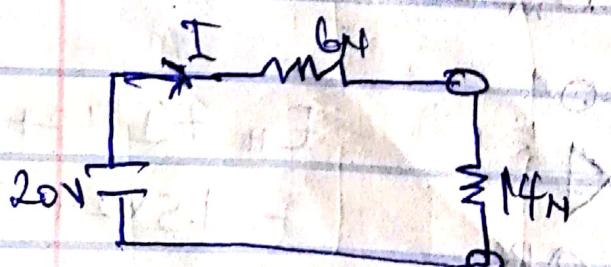


$$V_{14N} = 20 \times \frac{14}{6+14}$$

$$= 14V$$


$$I = \frac{20}{6+14} = 1A$$

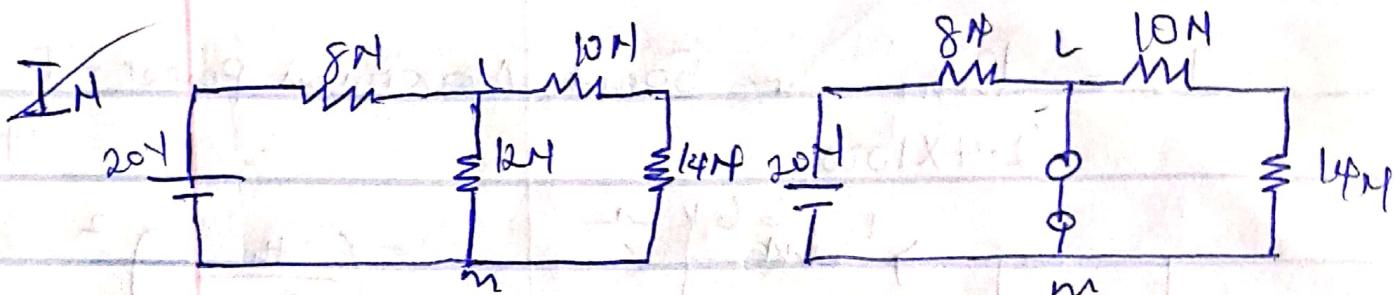

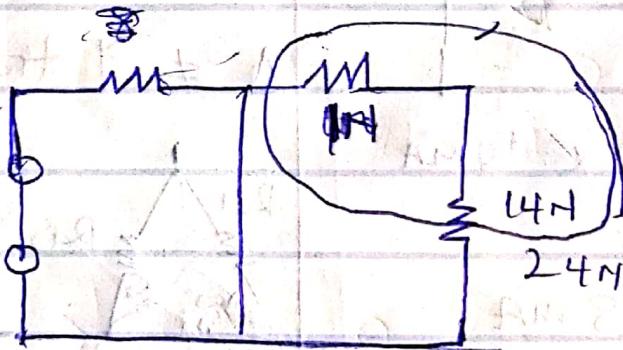
$$I_N = \frac{20}{8+12} = 2.5 \text{ A}$$



$$R_{th} = 8 // 24 = 6 \Omega$$

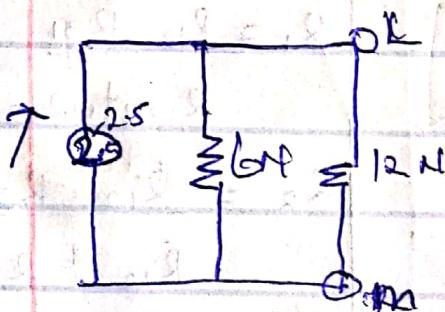
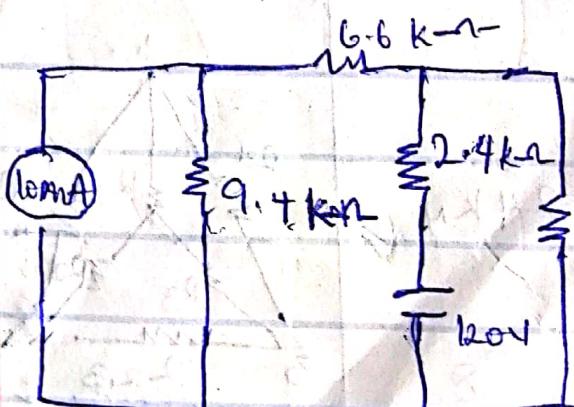
$$I_{12\Omega} = \frac{6}{6+12} \times 2.5 = 0.833 \text{ A}$$




$$I_N = I_1 + I_2$$


$$I_N = 5.8 \text{ mA} + 5.0 \text{ mA} \\ = 55.8 \text{ mA}$$

$$I_1 = \frac{9.4}{6.6 + 9.4} \times 10 \text{ mA} \\ = 5.8 \text{ mA}$$

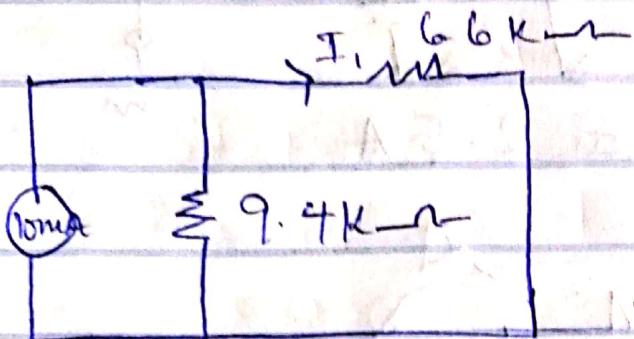
$$I_2 = \frac{120}{2.4 \times 1000} = 50 \text{ mA}$$


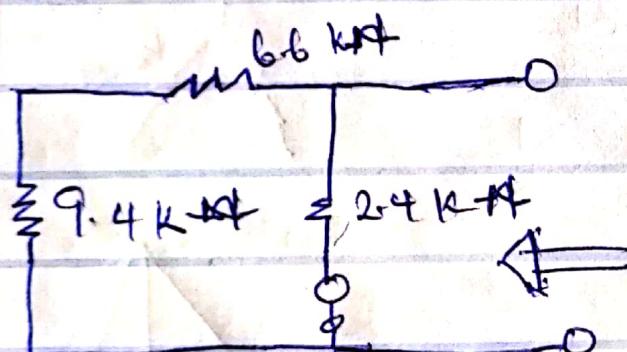
$$I_1 = \left(\frac{9.4}{6.6 + 9.4} \right) \times 10 \text{ mA} = 5.8 \text{ mA}$$


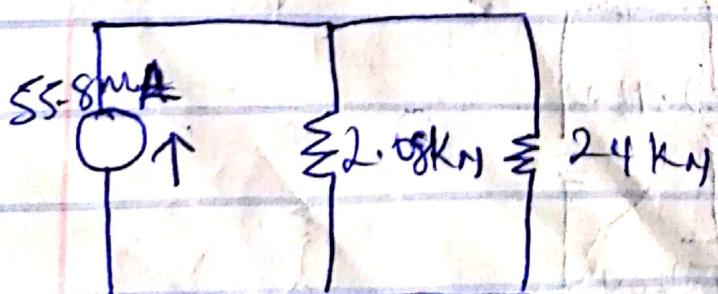
$$R_{th} = 2.4 / (9.4 + 6.6) = 2.08 \Omega$$




$$I_{24} = \frac{55.8 \times 2.08}{2.08 \times 24} = 4.45 \text{ A}$$

$$\text{Maximum Power} = \frac{E_{th}^2}{4R_L}$$

$$= \left(\frac{E_{th}}{R_L + R_s} \right)^2$$

$\Delta \neq Y$ transformation

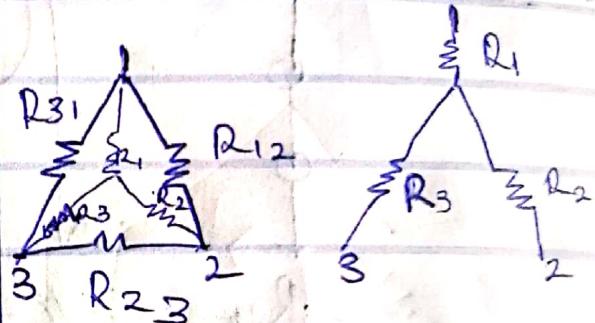


$$R_1 = R_{12} R_{31} / (R_{12} + R_{23} + R_{31})$$

$$R_2 = R_{12} R_{23} / (R_{12} + R_{23} + R_{31})$$

$$R_3 = R_{23} R_{31} / (R_{12} + R_{23} + R_{31})$$

$$R_{12} = R_1 R_2 + R_2 R_3 + R_3 R_1$$

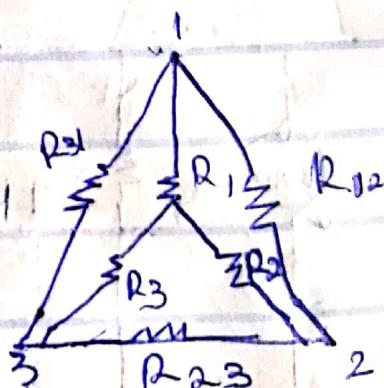

$$R_{12} = R_1 R_2 + R_2 R_3 + R_3 R_1 / R_3$$

$$R_{23} = R_1 R_2 + R_2 R_3 + R_3 R_1$$

$$R_{31} = R_1 R_2 + R_2 R_3 + R_3 R_1$$




$$R_{12} = R_1 R_2 + R_2 R_3 + R_3 R_1$$

$$R_{12} = \frac{12 \times 6 + 6 \times 8 + 8 \times 12}{8} = 27 \text{ N}$$

$$R_{23} = R_1 R_2 + R_2 R_3 + R_3 R_1$$



$$= \frac{12 \times 6 + 6 \times 8 + 8 \times 12}{12} = 18 \text{ N}$$

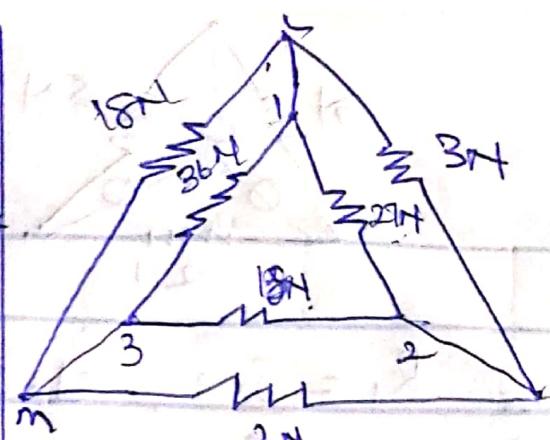
$$R_{31} = \frac{12 \times 6 + 6 \times 8 + 8 \times 12}{6} = 36 \text{ N}$$



$$\frac{27 \times 3}{27 + 3} = 27$$
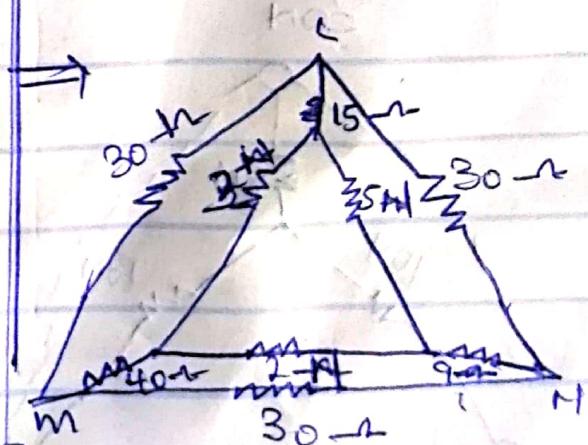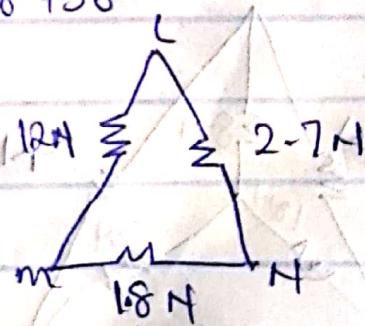
$$\frac{18 \times 36}{18 + 36} = 12 \text{ N}$$



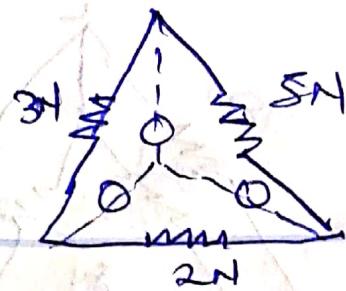



$$R_1 = \frac{5 \times 3}{5+2+3} = 1.5 \text{ N}$$

$$R_2 = \frac{2 \times 5}{5+2+3} = 1 \text{ N}$$

$$R_3 = \frac{3 \times 2}{5+2+3} = 0.6 \text{ N}$$

$$R_1 = 1.5 \text{ N}$$




$$R_2 = 1 \text{ N}$$

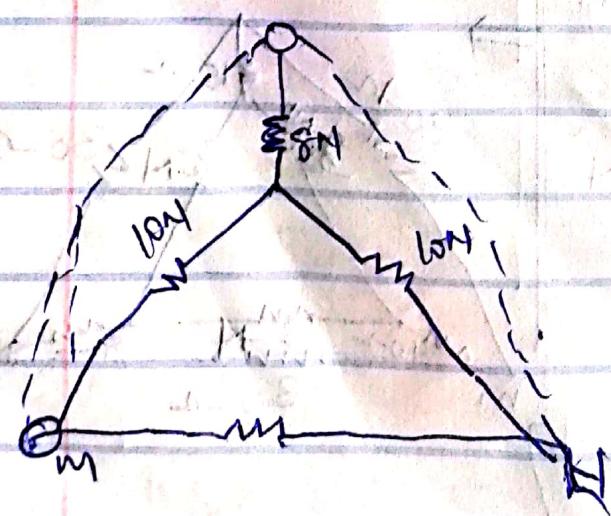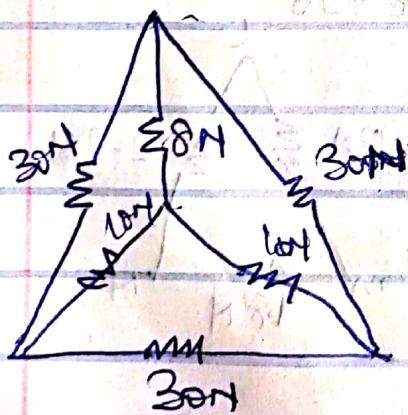

$$R_{12} = \frac{8 \times 10 + 10 \times 10 + 10 \times 8}{20} = 26 \text{ N}$$

$$R_{23} = \frac{8 \times 10 + 10 \times 10 + 10 \times 8}{8} = 32.5 \text{ N}$$
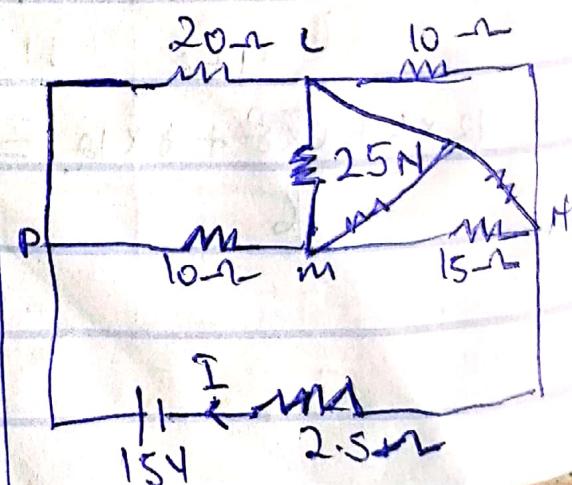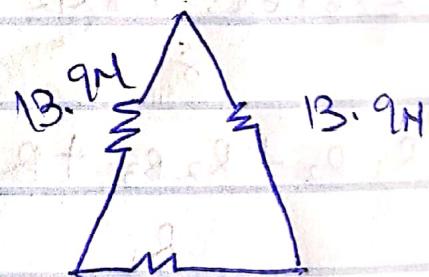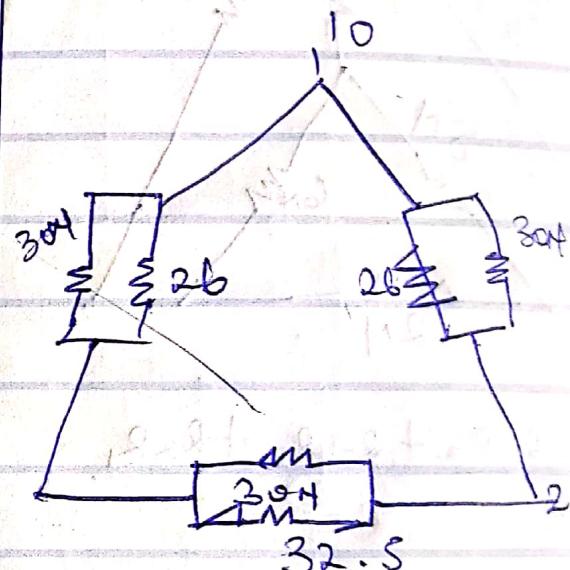
$$R_{31} = \frac{8 \times 10 + 10 \times 10 + 10 \times 8}{10} = 26 \text{ N}$$






the current

Find, (I) Supplied by the 15V battery using delta-star transformation.


$$R_1 = \frac{10 \times 25}{10 + 15 + 25}$$

$$R_2 = \frac{15 \times 10}{10 + 15 + 25}$$
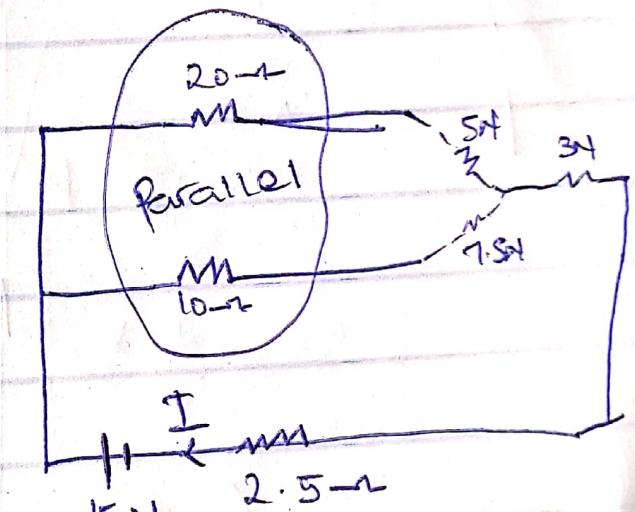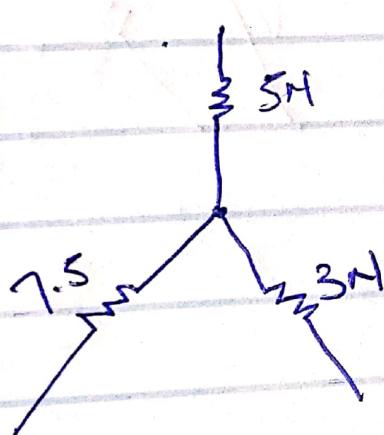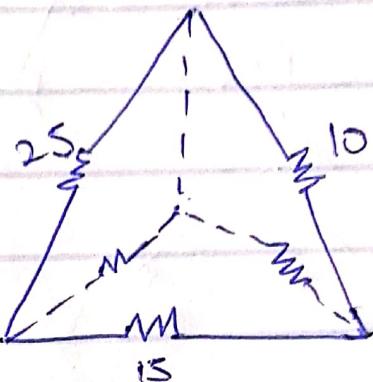
$$R_3 = \frac{25 \times 15}{10 + 15 + 25}$$



$$25 // 17.5 = 10.29 \Omega$$

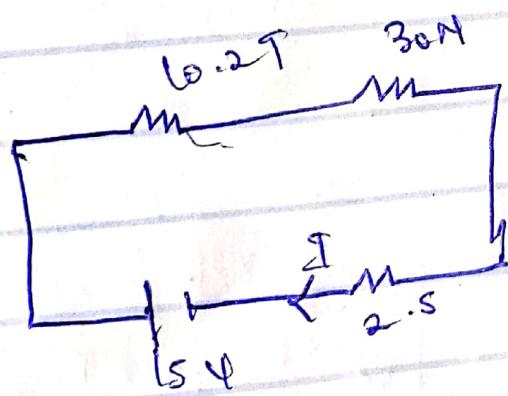

$$I = \frac{15}{15.29} = 0.95 A$$